

3 (a) State **one** similarity between *potential difference* and *electromotive force*.

.....
..... [1]

(b) Define the *volt*.

.....
..... [1]

(c) (i) Define the *kilowatt-hour* (kWh).

.....
..... [1]

(ii) Determine the value of the kilowatt-hour in joules.

1 kWh = J [1]

- (d) A d.c. supply is connected across a variable resistor. The resistance of the variable resistor is changed. Fig. 3.1 shows the variation of the power P dissipated in the resistance R of the variable resistor.

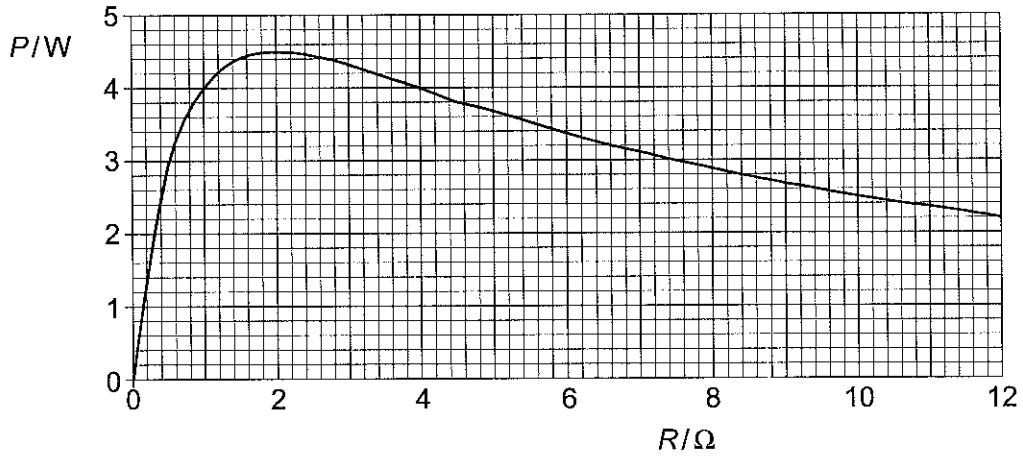


Fig. 3.1

- (i) Use Fig. 3.1 to determine the potential difference across the variable resistor when it dissipates maximum power.

potential difference = V [3]

- (ii) Explain why your answer to (i) is not equal to the e.m.f. of the supply.

.....

 [2]

[Total: 9]

3

- (a) Same unit / measured in volts / (both defined as) energy per (unit) charge / (both to do with) transfer of energy B1
- (b) 1 J (of energy transfer) per coulomb (of charge) (Allow 1 V = 1 JC⁻¹) B1
- (c)(i) It is the energy transferred by a 1 kW device working for 1 hour B1
- (c)(ii) 1 kWh = 1000 × 3600
1 kWh = 3.6 × 10⁶ (J) B1
- (d)(i) $P = \frac{V^2}{R}$ / $P = I^2 R$ / $I = 1.5$ (A) C1
 $4.5 = \frac{V^2}{2.0}$ / $V = 1.5 \times 2.0$ / $4.5 = 1.5 \times V$ C1
 potential difference = 3.0 (V) (Allow 1 sf) A1
 (Allow R in range 1.8 Ω to 2.2 Ω. This gives p.d. in the range 2.85 V to 3.15 V)
- (d)(ii) The supply has internal resistance B1
 There is also a p.d. across the internal resistance / 'lost volts' / energy wasted within the supply or internal resistance B1

[Total: 9]

4

- (a) Correct arrow(s) between the north and south poles B1
- (b) ~~current = $\frac{1.5}{8.0} = 0.1875$ (A) (Allow 0.19 A) C1~~
 ~~$F = 1.2 \times 10^{-2} \times 0.1875 \times 24$ (Current of 0.19 A gives 0.055 (N)) C1~~
~~force = 0.054 A1~~
~~unit: N / newton / TAm B1~~
- (c) The resistance of the wire *increases* by a factor of four (because $R \propto \frac{1}{A}$) / the current *decreases* by a factor of four B1
 Hence, the force decreases by a factor of four B1
 (Allow 1 mark for: Resistance is larger / current smaller and force smaller)

[Total: 7]

- 3 (a) In terms of energy transfers, state one major difference between electromotive force (e.m.f.) and potential difference (p.d.).

.....
 [1]

- (b) State one similarity between potential difference and electromotive force.

.....
 [1]

- (c) Fig. 3.1 shows two resistance wires X and Y connected in series to a battery.

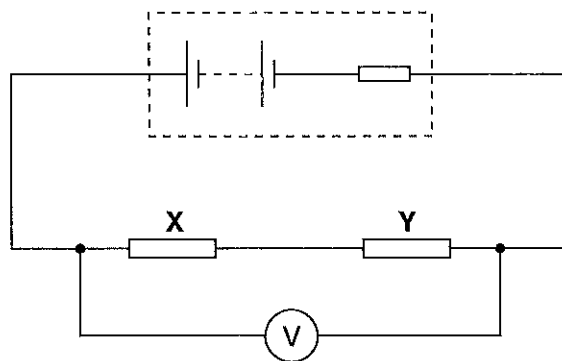


Fig. 3.1

- (i) The voltmeter has an infinite resistance. Explain why the voltmeter reading is not equal to the e.m.f. of the battery.

.....
 [1]

- (ii) The resistance of wire X is four times greater than the resistance of wire Y. The voltmeter reading is 6.0V. Use your knowledge of potential divider circuits to calculate the potential difference across the wire Y.

potential difference = V [3]

- (iii) The wires **X** and **Y** are connected in **parallel** to the battery. Explain which of the two wires will dissipate greater power.

.....
.....
..... [2]

[Total: 8]

Question	Expected Answers	Marks	Additional Guidance
3 a	For p.d. Charge(s) / electron(s) lose energy / change electrical energy to another form Or For e.m.f. Charge(s) / electron(s) gain energy / change energy to electrical energy	B1	
b	Both (have the same unit) volts / V / J C ⁻¹	B1	Allow Both 'energy/charge' (1) Do not allow the word "voltage(s)"
c i	There is p.d. across the internal resistor / resistance.	B1	Allow 'Energy / power lost in internal resistor / resistance' (1) Allow p.d. / voltage is used across the internal resistance.
ii	$V_{out} = \left(\frac{R_2}{R_1 + R_2}\right)V_{in}$ / $\frac{V_1}{V_2} = \frac{R_1}{R_2}$ $(V_{out}) = \frac{R}{R + 4R} \times 6.0$ / $(V_{out}) = \frac{1}{5} \times 6.0$ p.d. = 1.2 (V)	C1 C1	Allow 'Voltage splits in the ratio 4:1 (for X and Y)' for the first mark Allow 2 marks if second equation is written
iii	Wire Y Justified in terms of $P = \frac{V^2}{R}$ or $P \propto I/R$	M1 A1	Bald 1.2 V scores 3 marks Special case Allow 2/3 marks if the p.d. of 4.8 V is determined for X
Total		8	

5 (a) State Ohm's law.

.....

[2]

(b) From the list below, circle the quantity that is conserved in Kirchhoff's second law.

- charge e.m.f. energy time [1]

(c) Fig. 5.1 shows an electrical circuit.

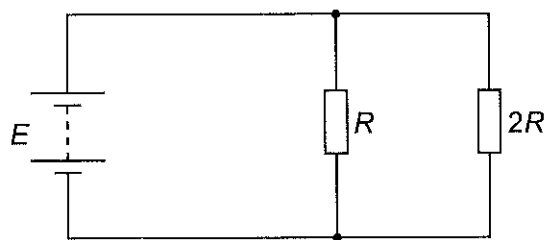


Fig. 5.1

The battery has e.m.f. E and negligible internal resistance. The resistances of the resistors are R and $2R$. Calculate

(i) the total resistance of the circuit in terms of R

resistance =[2]

(ii) the current from the battery in terms of E and R .

current =[1]

(d) Fig. 5.2 shows a circuit.

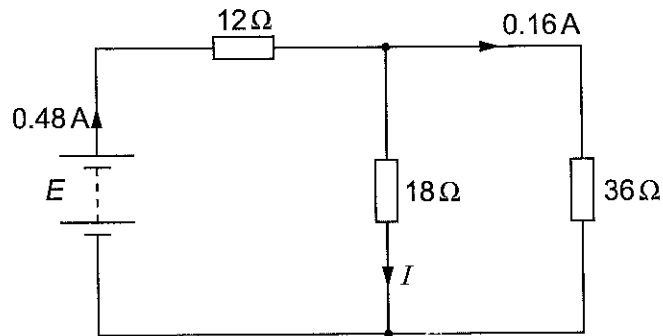


Fig. 5.2

The battery has negligible internal resistance.

Determine

(i) the charge passing through the battery in a time of 150 s

charge = C [2]

(ii) the number of electrons responsible for the charge in (i)

number = [1]

(iii) the current I in the $18\ \Omega$ resistor

current = A [1]

(iv) the e.m.f. E of the battery.

e.m.f. = V [2]

[Total: 12]

Please turn over for question 6.

5

- (a) The current is (directly) proportional to the p.d. / voltage
as long as the temperature remains constant (Allow 'physical conditions')
- (b) Only 'energy' is circled
- (c)(i) $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$
 $\frac{1}{R_{(t)}} = \frac{1+2}{2R}$
 $R_{(t)} = \frac{2R}{3}$ / resistance = 0.67 R
- (c)(ii) current = $\frac{3E}{2R}$ / current = $\frac{1.5E}{R}$ / current = $\frac{E}{2/3R}$ (Possible ecf)
- (d)(i) $Q = It$
 $Q = 0.48 \times 150$
charge = 72 (C)
- (d)(ii) number (= $\frac{72}{1.6 \times 10^{-19}}$) = 4.5×10^{20} (Possible ecf)
- (d)(iii) current = 0.32 (A)
- (d)(iv) total resistance of 18 Ω and 36 Ω in parallel = 12 Ω
total resistance of circuit = 12 + 12 = (24 Ω)
 $E = 0.48 \times 24$
e.m.f. = 11.52 (V) \approx 12 (V)
- Or
- $V_{12} = 0.48 \times 12 (= 5.76)$ / $V_{18} = 18 \times 0.32 (= 5.76)$ / $V_{36} = 36 \times 0.16 (= 5.76)$
 $E = 5.76 + 5.76$
e.m.f = 11.52 (V) \approx 12 (V)

[Total: 12]

- 3 A negative temperature coefficient (NTC) thermistor is connected across the terminals of a battery of e.m.f. 6.0V and of negligible internal resistance. Fig. 3.1 shows the variation of current I with time t from the moment the thermistor is connected to the battery.

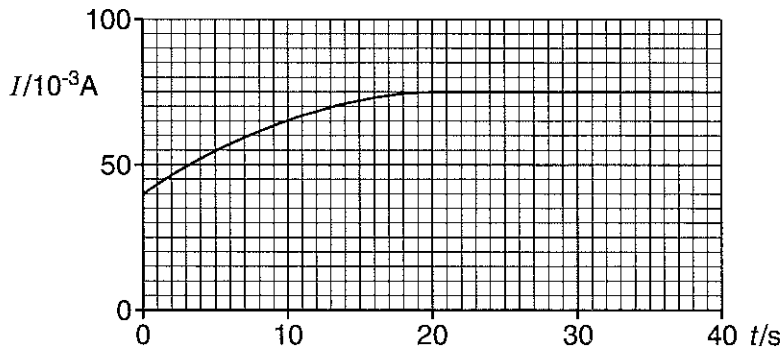


Fig. 3.1

- (a) Calculate the power dissipated by the thermistor at time $t = 0$.

power = W [2]

- (b) In this question two marks are available for the quality of written communication.

Explain the shape of the graph of Fig. 3.1.

.....

.....

.....

.....

.....

.....

.....

.....

.....

..... [4]

Quality of Written Communication [2]

[Total: 8]

Answer **all** the questions.

1 A cell, a resistor of resistance 120Ω and a negative temperature coefficient (NTC) thermistor are connected in **series**.

(a) In the space below, sketch a circuit diagram of this arrangement.

[2]

(b) The cell has e.m.f. 1.4V and negligible internal resistance. At a particular temperature, the current in the resistor is $5.0 \times 10^{-3}\text{A}$.

(i) Calculate the potential difference across the resistor.

potential difference =V [2]

(ii) Calculate the resistance of the thermistor at this temperature.

resistance = Ω [2]

(c) State and explain how the potential difference across the resistor changes when the temperature of the thermistor is lower.

.....
.....
..... [2]

[Total: 8]

1

- (a) Correct symbols for the cell (not battery), resistor and thermistor B1
Correctly drawn circuit B1
- (b)(i) $V = IR$ / $V = 0.005 \times 120$ C1
potential difference = 0.60 (V) (Allow 1 sf) A1
- (b)(ii) $V = 1.4 - 0.6 (= 0.8 \text{ V})$ (Possible ecf) C1
 $R = \frac{0.8}{0.005}$
resistance = 160 (Ω) A1
[Allow 1 mark for total resistance calculation: $R = 1.4 / 0.005 = 280$ (Ω)]
- (c) The resistance of the thermistor increases / the current decreases B1
Hence, the p.d across the resistor decreases. B1

[Total: 8]

2

- (a) All 4 graphs identified correctly B1
- (b)(i) The resistance / R remains constant B1
 $I \propto V$ / Graph has a constant slope / gradient / Obeys Ohm's law B1
- (b)(ii) R is infinite / large when: $I = 0$ / no conduction / 'reverse' direction / 'up to a point' / negative V / negatively biased B1
 R is small / decreases / low(er) when: I is not zero / there is conduction / 'positive' direction / 'beyond a point' / positive V / positively biased B1
(No credit for 'conducts in one direction only')
- (b)(iii) The resistance increases as I (or V) increases B1
The temperature increases (as I increases) / more electrons collisions (with the vibrating atoms / ions) B1

QWC

The answer must involve physics, which attempts to answer the question.

Structure and organisation -

Award this mark if the whole answer is well structured. B1

Spelling and Grammar mark -

More than two spelling mistakes or more than two grammatical errors means the SPAG mark is lost. B1

[Total: 9]

- 3 Fig. 3.1 shows a circuit consisting of a battery of electromotive force 16.0V and negligible internal resistance, two resistors and a thermistor.

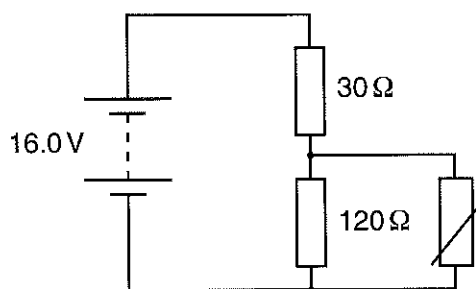


Fig. 3.1

- (a) (i) Define the term *electromotive force* (*e.m.f.*).

.....

 [2]

- (ii) Explain the meaning of the term *internal resistance*.

.....

 [1]

- (b) The thermistor has a resistance of $360\ \Omega$ at 20°C . Calculate

- (i) the total resistance R of the thermistor and the resistor of resistance $120\ \Omega$ at 20°C

$$R = \dots\dots\dots \Omega \text{ [2]}$$

- (ii) the potential difference V across the thermistor.

$$V = \dots\dots\dots \text{ V [3]}$$

- (iii) It is suggested that the thermistor in the circuit of Fig. 3.1 is used to monitor temperatures between 20°C and 200°C. Describe how the potential difference across the thermistor and the current in it will vary as the temperature increases above 20°C.



In your answer you should explain why the potential difference and current vary as the temperature increases.

.....
.....
.....
.....
.....
.....
..... [4]

- (c) The battery in Fig. 3.1 is rechargeable.

- (i) Calculate the charge stored in the battery when it is charged for 8.0 hours at a constant current of 1.2A.

charge = unit [3]

- (ii) After charging, the battery loses energy at a constant rate of 1.4Js⁻¹. The e.m.f. of the battery remains constant at 16.0V. Calculate how many hours it takes for the battery to discharge.

discharge time = h [3]

[Total: 18]

Question			Answer	Marks	Guidance
3	(a)	(i)	energy transferred from source/changed from some form to electrical energy; per unit charge (to drive charge round a complete circuit)	M1 A1	allow chemical
		(ii)	(some) energy is transferred into thermal energy /lost as heat in (driving charge through) the battery. It behaves as if it has an (internal) resistance/AVV or there is a voltage drop across/decrease in voltage from the battery when a current is drawn from it/AVV	B1	allow any description which uses $E = V + Ir$ with symbols defined but not just the formula alone or e.g. statement about 'lost volts'/current
	(b)	(i)	correct substitution into resistors in parallel formula $R = 90 \Omega$	C1 A1	$1/R = 1/90$ or 0.011 correct answer
		(ii)	using $V_{out} = R_2/(R_1 + R_2) V_{in}$: alt: $16 = I \times 120$ $V_{out} = 90/(30 + 90) 16$ so $I = 0.133 \text{ A}$ $V_{out} = 12 \text{ V}$ $V_{out} = 0.13 \times 90 = 12 \text{ V}$	C1 C1 A1	ecf (b)(i) accept $V_{out} = (90/120) \times 16 = 12 \text{ V}$ for full marks N.B. beware of false ratios, e.g. $360/(120 + 360)$ giving correct answer; give first marking point only
A A A		(iii)	resistance (of thermistor) decreases (with temperature increase) current <u>in circuit</u> increases or as <u>total</u> resistance is less so current in thermistor increases voltage ratio between 30Ω and combination changes so voltage across thermistor falls	B1 M1 A1 M1 A1	max 4 marks QWC mark is either of the M marks
	(c)	(i)	$Q = It = 1.2 \times 8 \times 60 \times 60$ $Q = 34560 \text{ (C)}$ correct unit,	C1 A1 B1	accept 3.5 or 3.46×10^4 allow 1 mark for answer of 9.6 or 576 allow C, kC, A s; N.B. 9.6 A h or 576 A min score 3/3
		(ii)	energy = $34560 \times 16 = 552960 \text{ J}$ or $I = 1.4/16 = 0.0875 \text{ A}$ time = $552960/1.4 = 394970 \text{ s}$ then $t = 34560/I$ time = $394970/3600 = (109.7 \text{ h}) = 110 \text{ h}$	C1 C1 A1	ecf (c)(i) allow full marks for $1.2 \times 8 \times 16/1.4 = 110 \text{ h}$ allow 111 h when using $3.5 \times 10^4 \text{ C}$
Total				18	

- 2 (a) The battery in an electric car has an e.m.f. of 24V. It can provide a current of 200A to the motor for a period of 4.0 hours.

(i) Define the term *electromotive force* (e.m.f.) for the battery.

.....

 [2]

(ii) Show that the total charge Q that can be delivered by the battery is about 3×10^6 C.

[2]

(iii) Calculate the total energy E that can be supplied by the battery at a constant e.m.f. of 24V.

$$E = \dots\dots\dots \text{ J [2]}$$

- (b) The charger for the battery has a 30V output supplying a current I . The total resistance of the circuit is indicated by one resistor R in Fig. 2.1. The positive terminal of the battery is connected to X.

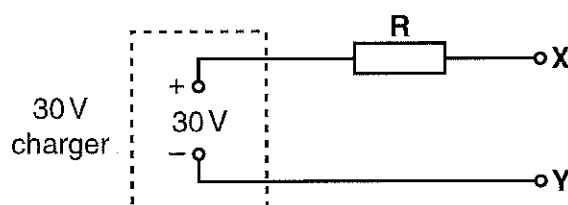


Fig. 2.1

(i) Complete the circuit by drawing the correct symbol for the battery between X and Y on Fig. 2.1. The battery has negligible internal resistance. [1]

(ii) The potential difference across the battery remains at 24V. The current I provided by the battery charger is constant at 120 A. Show that the value of the resistance of R is 0.050Ω .

[2]

- (iii) Calculate the power lost in **R** as the battery is charging.

power lost = W [2]

- (iv) The efficiency of the charging process is given by the equation

$$\text{efficiency} = \frac{\text{input power from charger} - \text{power loss in R}}{\text{input power from charger}}$$

Calculate its value as a percentage.

efficiency = % [3]

- (c) (i) Show that it takes about 7 hours to charge a completely flat battery.

[2]

- (ii) Calculate the cost of charging the battery at 26p per kWh.

cost = p [1]

[Total: 17]

Question		Answer	Marks	Guidance
2	(a) (i)	energy transfer per unit charge from chemical/other to electrical form	B1 B1	allow energy per unit charge
	(ii)	$(Q = It) = 200 \times 4 \times 60 \times 60$ $= 2.9 \times 10^6 \text{ (C)}$	M1 A1	accept 200×14400 accept 2.88×10^6
	(iii)	$E = QV = 2.88 \times 10^6 \times 24$ $= 6.9 \times 10^7 \text{ (J)}$	C1 A1	accept 72 MJ if using 3 MC or 69.6 or 70 if using 2.9 MC
	(b) (i)	correct symbol and polarity connected to X and Y	B1	allow one cell or more or two cells with dotted lines between
A A A	(ii)	$V = 30 - 24 = 6 \text{ V}$ $R = V/I = 6/120$ $= 0.05 \text{ (}\Omega\text{)}$	M1 M1 A0	evidence of the V subtraction needed do not allow use of $E = V + Ir$; it must be IR
	(iii)	$P = VI = 6 \times 120$ $= 720 \text{ (J s}^{-1}\text{)}$	C1 A1	or $I^2R = 120^2 \times 0.05$ or $V^2/R = 6^2 / 0.05$
	(iv)	$(3600 - 720)/3600 = 2880/3600$ $= 0.8$ $= 80 \text{ (\%)}$	C1 C1 A1	ecf b(iii); using 2880 instead of 3600 gives 75%; scores zero allow $(30 - 6)/30I = 24/30 = 0.8 = 80 \text{ (\%)}$
	(c) (i)	$t = Q/I = 2.88 \times 10^6/120$ or $E/VI = 69 \times 10^6/(24 \times 120)$ $t = 2.4 \times 10^4/3600 = 6.7 \text{ h}$	M1 A1	ecf (a)(iii); accept 3×10^6 giving $2.5 \times 10^4 \text{ s}$ and 6.9 h allow ora using 7.0 h giving $E = 72.5 \text{ MJ}$
	(ii)	power supplied $= 30 \times 120/1000 = 3.6 \text{ kW}$ cost $= 3.6 \times 7 \times 26 = 655 \text{ (p)}$	A1	ecf c(i) accept any consistent answer do not allow 2.88 kW giving 524 p unless repeated error from b(iv)
		Total	17	

Answer **all** the questions.

- 1 Fig. 1.1 shows the I – V characteristic of a slice of semiconducting material.

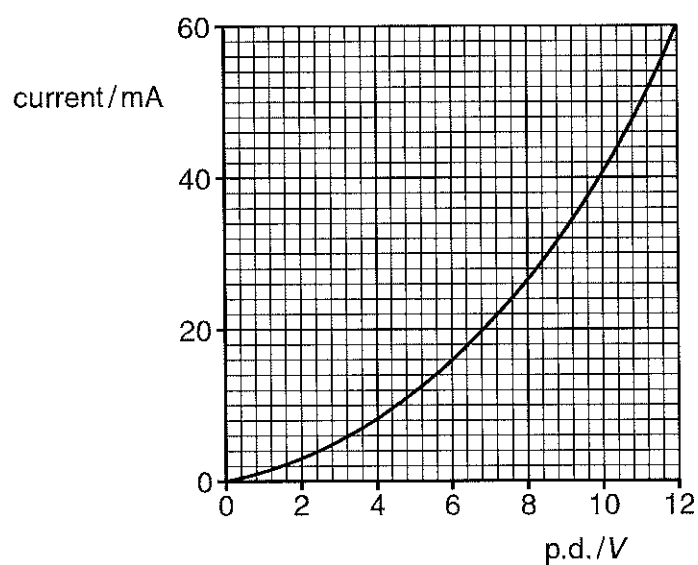


Fig. 1.1

- (a) (i) Define *resistance*.

.....
 [1]

- (ii) Show that the resistance of the slice is about $250\ \Omega$ when there is a current of 40 mA in it.

[2]

- (b) The dimensions of the slice are shown in Fig. 1.2.

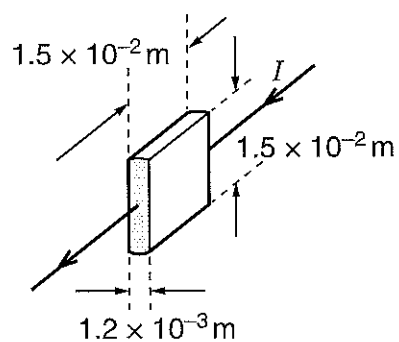


Fig. 1.2

Calculate the resistivity ρ of the semiconducting material when there is a current I of 40 mA in the slice.

$\rho = \dots\dots\dots \Omega \text{ m}$ [3]

- (c) Explain how the $I-V$ characteristic shows that the resistivity of the semiconducting material decreases with increasing temperature.



In your answer you should explain how you are aware that the temperature of the slice changes.

.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....
.....

[4]
[Total: 10]

Question			Answer	Marks	Guidance
1	(a)	(i)	potential difference (across a component)/current (in it)	B1	allow symbols if symbols defined; voltage or p.d.; allow per not over
		(ii)	read 10 V from graph ($R = V/I = 10/0.04$ $= 250 \text{ } (\Omega)$)	C1 M1 A0	allow 9.8 or 9.9 ecf reading from graph
	(b)		$R = \rho l/A$ or $\rho = RA/l$ $\rho = 250 \times 1.2 \times 10^{-3}$ $\rho = 0.30 \text{ } (\Omega \text{ m})$	C1 C1 A1	select formula mark ecf(a)(ii) ; a correct substitution correct answer allow 0.3
A A A	(c)		(graph curves so) R changes qualification: I increases faster than V increased temperature is caused by (larger) current in slice qualification: $P = I^2R$ as R decreases ρ decreases	B1 B1 B1 B1 B1	allow R increases or decreases allow : by calculating two values of R do not allow either of the first two marking points if reference made linking gradient and R value QWC mark ; allow heating effect is caused by.... allow 'R decreases' already stated earlier in answer max 3 out of 4 + QWC mark
Total				10	

3 A cell is a source of e.m.f. When the cell is connected into a circuit the potential difference measured between its terminals, called the *terminal p.d.*, is less than its e.m.f.

(a) (i) Define the term *e.m.f.*

.....

 [2]

(ii) Explain why the terminal p.d. is less than the e.m.f.

.....

 [2]

(b) In the circuit of Fig. 3.1 the cell of e.m.f. 1.6V and internal resistance r is delivering a current of 0.20A to a resistor of resistance R . The voltmeter reads the terminal p.d. It is 1.2V.

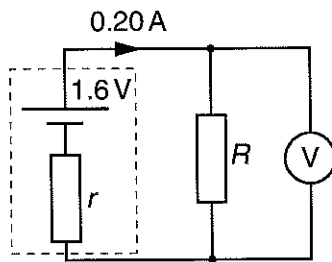


Fig. 3.1

Calculate the values of

(i) the resistance R

$R = \dots\dots\dots \Omega$ [2]

(ii) the internal resistance r .

$r = \dots\dots\dots \Omega$ [2]

(c) (i) The current in the resistor of Fig. 3.1 remains constant at 0.20A for several hours. Calculate

1 the charge which passes through the resistor in 1.5 hours

charge = unit [3]

2 the energy dissipated by the resistor in 1.5 hours.

energy = J [2]

(ii) The cell is left connected to the resistor for 12 hours. The graph of Fig. 3.2 shows the variation of current I with time t .

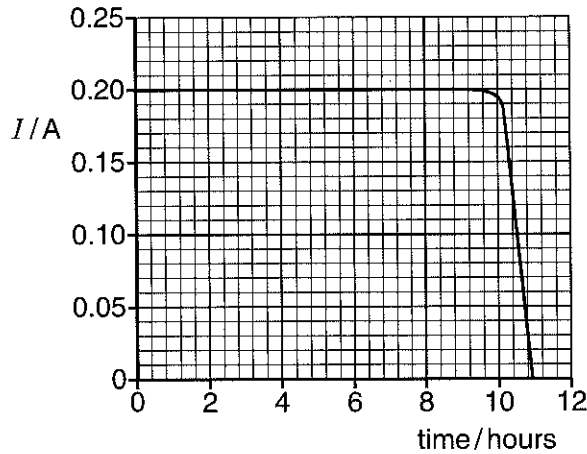


Fig. 3.2

Describe how the current varies with time. Suggest reasons why it varies in this way.



In your answer you should link each feature of the graph to the reason for it.

.....

.....

.....

.....

.....

.....

.....

..... [4]

[Total: 17]

Turn over

Question			Answer	Marks	Guidance
3	(a)	(i)	energy transferred from source/changed from some form to electrical energy; per unit charge (to drive charge round a complete circuit)	M1 A1	allow energy <u>divided by</u> charge
		(ii)	any source has an <u>internal resistance</u> where energy is transferred into thermal energy /lost as heat	B1 B1	there will be 'lost' volts (across the cell when a current is drawn) or $V = E - Ir$ explained
	(b)	(i)	$V = IR$ $1.2 = 0.2 R$ $R = 6.0 \Omega$	C1 A1	substitution needed to score mark allow 6Ω
		(ii)	$1.6 - 1.2 = 0.4 = 0.2 r$ $r = 2.0 \Omega$	C1 A1	allow 2Ω
	(c)	(i)1	$Q = It = 0.20 \times 3600 \times 1.5$ $= 1100$ correct unit,	C1 A1 B1	substitution needed to score mark 1080 allow 1 mark max for 0.3 or 18 allow C, kC, A s exception 0.3 A h or 18 A min scores 3 marks
		(i)2	energy = $QV = 1100 \times 1.2$ or $I^2Rt = 0.2^2 \times 6 \times 5400$ $= 1320$ (J)	C1 A1	ecf (c)(i)1 substitution needed to score mark 1296(1080) allow 1 mark for 1728 (using 1.6)
		(ii)	I is constant for about 9 to 10 hours because <u>internal</u> resistance remains constant/cell operates at constant <u>emf</u> I falls <u>rapidly/towards zero</u> over last hour or so because <u>cell's/chemical energy</u> is used up (so E falls)	B1 B1 B1 B1	QWC must have link between observation and reason to score full marks accept r of cell increases causing fall in V or I
Total				17	

- 2 This question is about possible heating circuits used to demist the rear window of a car. The heater is made of 8 thin strips of a metal conductor fused onto the glass surface. Fig. 2.1 shows the 8 strips connected in parallel to the car battery of e.m.f. E and internal resistance r .

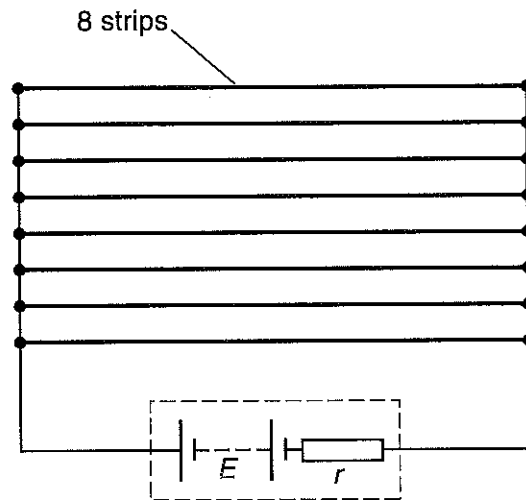


Fig. 2.1

- (a) The potential difference across each strip is 12V when a current of 2.0A passes through it.

- (i) Calculate the resistance r_p of one strip of the heater.

$$r_p = \dots\dots\dots \Omega \text{ [1]}$$

- (ii) Calculate the total resistance R_p of the heater.

$$R_p = \dots\dots\dots \Omega \text{ [3]}$$

- (iii) Show that the power P dissipated by the heater is about 200W.

[2]

- (b) Each strip is 0.90m long, 2.4×10^{-4} m thick and 2.0×10^{-3} m wide.

Calculate the resistivity ρ of the metal of the strip. Give the unit with your answer.

$$\rho = \dots\dots\dots \text{unit} \dots\dots\dots \text{ [4]}$$

(c) An alternative way of making the heater is to connect eight metal strips in **series**. The heater is to dissipate the same power as the parallel combination of (a) when the p.d. across it is 12V.

(i) Explain why the total resistance of the series heater must equal R_p calculated in (a)(ii).

.....
 [1]

(ii) Calculate the resistance r_s of one strip of this series heater.

$r_s = \dots\dots\dots \Omega$ [1]

(iii) Suggest, with a reason, whether you would choose the series or parallel circuit arrangement of the strips for a demister heater.

.....
 [1]

(d) Fig. 2.2 is a graph showing how the potential difference across the terminals of the battery varies with the current drawn from it.

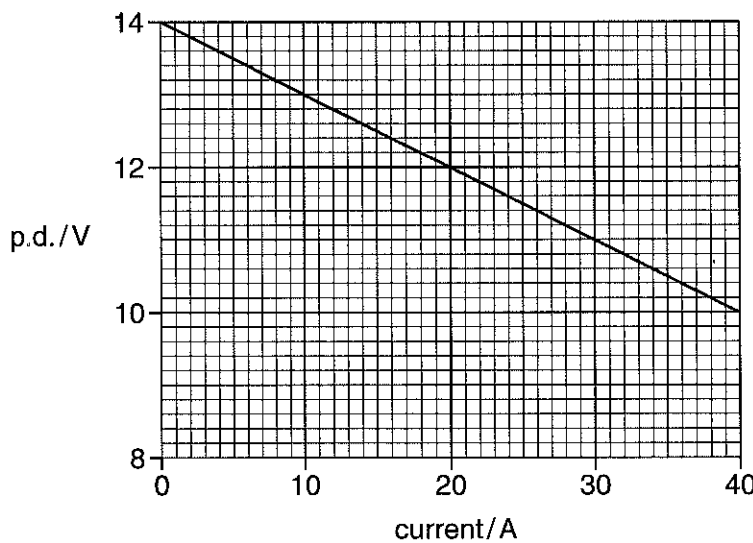


Fig. 2.2

(i) From the graph find the e.m.f. E of the battery.

$E = \dots\dots\dots V$ [1]

(ii) Use data from the graph to calculate the internal resistance r of the battery.

$r = \dots\dots\dots \Omega$ [3]

[Total: 17]

Turn over

Question	Expected Answers	M	Additional Guidance
2			
a	i		
	ii		
	iii		
b			
c	i		
	ii		
	iii		
d	i		
	ii		
Total question 2		17	

- 2 (a) A 12V car battery contains an electrolyte. The battery is connected to an electric motor **M**. There is a current in the motor and the battery. See Fig. 2.1.

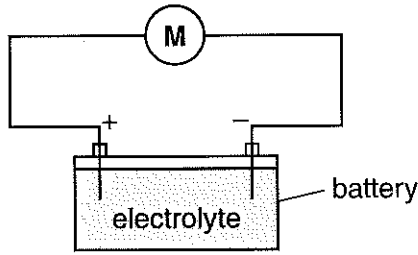


Fig. 2.1

State

- (i) the charge carriers in the electrolyte
 [1]
 - (ii) the charge carriers moving through the electrolyte to the positive terminal of the battery
 [1]
 - (iii) the charge carriers moving through the wires to the positive terminal of the battery.
 [1]
- (b) When used to start the engine of the car, the electric motor draws 40A from the battery of e.m.f. 12V. The potential difference across the motor at this time is only 8.0V.
- (i) Explain why the potential difference across the motor at this time is not the same as the e.m.f. of the car battery.

 [2]
 - (ii) Show that the internal resistance of the battery is 0.10Ω .

[3]

- (iii) It takes 1.2s for the electric motor to start the engine. Calculate the charge Q which passes through the electric motor in this time.

$Q = \dots\dots\dots$ C [2]

- (c) The car has two 12V headlamps each rated at 54W, connected in parallel to the battery. In normal working conditions the current in each lamp is 4.5A.

- (i) Explain how and why the resistance of the headlamp filament varies with the current passing through it.

.....
.....
.....
.....
..... [2]

- (ii) Suggest a value for the current rating of a fuse for the headlamp circuit. Justify your choice.

.....
.....
..... [2]

- (iii) A car contains a number of different fuses for its various electrical circuits. Suggest why this is necessary.

.....
.....
..... [1]

[Total: 15]

Question			Expected Answers	M	Additional Guidance
2	a	i	ions	B1	
		ii	positive ions	B1	allow positive charges / cations
		iii	electrons	B1	
b	i	i	the battery has an internal resistance/AW some of the emf is across the (internal) resistance (leaving a smaller p.d. across motor)	B1 B1	accept connecting leads have resistance accept $V = E - Ir$ or 'lost volts'/p.d. across r
		ii	use $E = V + Ir$ giving $12 = 8 + 40r$ $r = (12 - 8)/40$ or $4/40$ $= 0.10 \Omega$	C1 M1 M1 A0	accept reverse solution, $0.10 \Omega \rightarrow 8 V \rightarrow 12 V$ substitution and or solution showing working
		iii	$Q = It = 40 \times 1.2$ $I = 48 (C)$	C1 A1	
c	i	i	The current heats the filament The resistance/resistivity (of the metal filament) increases (with temperature).	B1 B1	no mention of temperature increase or heating scores zero
		ii	4.5 to 8 A in <u>each (parallel) arm</u> or 9 to 16 A for both together needs to be great enough to cover initial surge/current or use antisurge fuses	B1 B1	no mark if fuse value outside range
		iii	e.g. the starter motor draws 40 A so would need a bigger fuse than headlamp circuit so need different fuses for different situations or if battery used for starter motor with lights on will need too large a fuse – damage occurs before fuse blows/AW	B1	accept headlamp circuit damaged before fuse blows if 40 A fuse only used or fuse blows in starter circuit if 10 A used, etc.
Total question 2				15	

- 3 (a) The following electrical quantities are often used when analysing circuits. Draw a straight line from each quantity on the left-hand side to its correct units on the right-hand side.

potential difference	Cs^{-1}
resistance	JC^{-1}
power	VA^{-1}
current	Js^{-1}

[3]

- (b) Fig. 3.1 shows a battery of e.m.f. 6.0V and negligible internal resistance connected in series with a thermistor and a $560\ \Omega$ resistor.

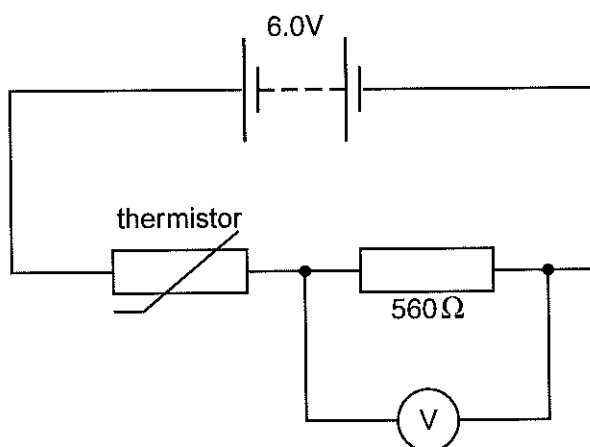


Fig. 3.1

The voltmeter across the resistor has infinite resistance.

- (i) The reading on the voltmeter is 2.4V. Calculate the resistance R_T of the thermistor.

$$R_T = \dots\dots\dots \Omega \text{ [3]}$$

- (ii) Calculate the current in the circuit.

$$\text{current} = \dots\dots\dots \text{ A [1]}$$

(c) The variation of resistance with temperature for this thermistor is shown in the graph of Fig. 3.2.

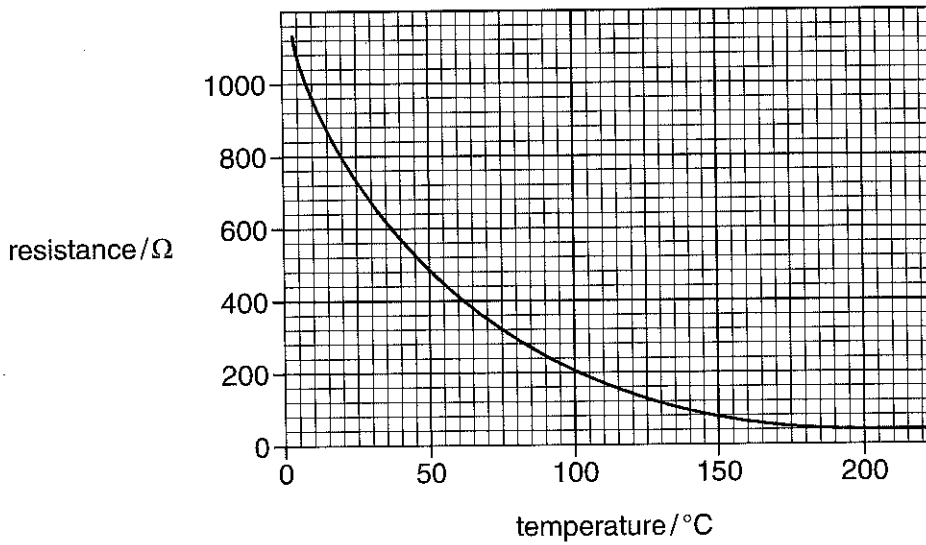


Fig. 3.2

(i) Use the graph to determine the temperature of the thermistor when its resistance is 800 Ω.

temperature = °C [1]

(ii) State and explain, without calculation, how the reading of the voltmeter in Fig. 3.1 will change as the temperature of the thermistor increases to 80 °C.

.....

.....

.....

.....

..... [3]

- (iii) The circuit of Fig. 3.1 can be used as a temperature sensor. Temperature sensors are used in the kitchen to control the internal temperatures of ovens (typically 200°C) and refrigerators (typically 4°C). Use the graph of Fig. 3.2 to suggest in which device this sensor would be more suitable.



In your answer you should link the information from the graph to the working of the sensor.

.....

.....

.....

.....

.....

..... [3]

[Total: 14]

Question		Expected Answers	M	Additional Guidance	
3					
a	i	$V \quad J C^{-1}$ $R \quad V A^{-1}$ $P \quad J s^{-1}$ $I \quad C s^{-1}$	B1 B1 B1	4 correct 3 marks; 2 correct 2 marks 1 correct 1 mark	
b	i	using $V_{out} = R_2/(R_1 + R_2) V_{in}$: $V_{out} = 3.6 V$ $3.6 = R_2/(560 + R_2) 6$ $R_2 = 840 (\Omega)$	alt: $2.4 = I \times 560$ so $I = 4.3 \text{ mA}$ $3.6 = I R_2$	C1 C1 A1	accept $R_2 = (3.6/2.4) \times 560$ or $2.4 = 560/(560 + R_2) 6$
	ii	$I = 4.3 \times 10^{-3} (A)$	B1	accept 4.3 m(A) or $3/700 (A)$ ecf (b)(i) i.e. $I = 6/(560 + R_2)$	
c	i	$20 \pm 2 (^\circ C)$	B1		
	ii	R_{Th} will fall/ resistance will fall giving greater share of supply V across fixed R/AW causing the voltage across (fixed) $R/voltmeter$ reading to rise	B1 B1 B1	accept explanation in terms of potential divider equation or current increases or current same in both resistors/resistors in series	
	iii	ΔR is large for small ΔT at low temperatures/ AW in terms of gradient so thermistor is better in circuit to control low temp, refrigerator	M2 A1	accept sensitivity greater at low temperature or vice versa or ΔR is small for small ΔT at high temperatures scores 1 out of 2	
Total question 3			14		

4 Fig. 4.1 shows part of a circuit where three resistors are connected together.

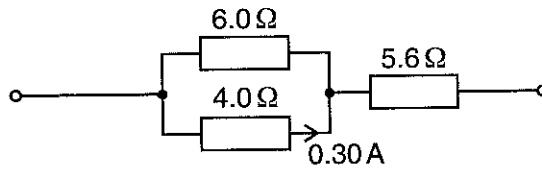


Fig. 4.1

The current in the $4.0\ \Omega$ resistor is $0.30\ \text{A}$.

(a) Explain why the current in the $6.0\ \Omega$ resistor is $0.20\ \text{A}$.

.....

.....

.....

.....

.....

..... [2]

(b) (i) State the law which enables you to calculate the current in the $5.6\ \Omega$ resistor.

.....

..... [1]

(ii) Calculate the current in the $5.6\ \Omega$ resistor.

current = A [1]

(c) Calculate the total resistance R of the combination of resistors.

$R =$ Ω [3]

(d) To cause the current of 0.30 A in the $4.0\ \Omega$ resistor, the resistor combination is connected to a d.c. supply of electromotive force (e.m.f.) 5.0 V.

(i) Explain the term *e.m.f.*

.....
.....
..... [2]

(ii) Show that the terminal potential difference across the supply is 4.0 V.

[1]

(iii) Calculate the internal resistance of the supply.

internal resistance = Ω [2]

[Total: 12]

Question		Answer	Marks	Guidance
4	(a)	R's in parallel have same V/AW so $4.0 \times 0.30 = 6.0 \times 0.20$	M1 A1	allow i splits in inverse ratio to R or AW; hence I in 6 ohm = $4 / 6 \times 0.3 = 0.2$ A
	(b) (i)	sum of total current into a junction equals the sum of total current out or total algebraic sum of currents is zero	B1	allow Kirchoff's first law
	(ii)	0.50 (A)	A1	accept 0.5 (A) (no SF error)
	(c)	correct formula for R_p and substitution $R_p = 2.4 \Omega$ $R_s = 8.0 (\Omega)$	C1 C1 A1	apply ecf to R_p for second mark accept 8 (Ω) (no SF error)
	(d) (i)	energy transferred from source/changed from some form to electrical energy; per unit charge (to drive charge round a complete circuit)	M1 A1	allow form as e.g. light/chemical/heat allow energy <u>divided by</u> charge
	(ii)	$V = IR = 0.50 \times 8.0 = 4.0$ (V)	A1	ecf b(ii),c i.e. answer = b(ii) x c accept 4 (V) (no SF error)
	(iii)	$E - V = Ir$ giving $5.0 - 4.0 = 0.50 r$ $r = 2.0 (\Omega)$	C1 A1	ecf b(ii) accept 2 (Ω) (no SF error); give max of 1 mark for $r = 3.3 \Omega$, i.e. using $I = 0.3$ A
		Total	12	

3 (a) A battery charger contains a microprocessor circuit so that it can charge an AA rechargeable cell at a constant current of 450 mA. It takes 4 hours 40 minutes to charge a 1.5V cell from a fully discharged state.

(i) Calculate the charge Q passing through the cell during the charging process.

$Q = \dots\dots\dots$ unit $\dots\dots\dots$ [3]

(ii) Fig. 3.1 shows the cell of internal resistance $0.90\ \Omega$ connected to the battery charger. Assume that the e.m.f. of the cell is 1.5V.

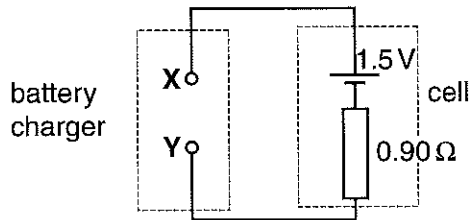


Fig. 3.1

1 State whether the terminal X of the battery charger is positive or negative.

.....

2 Mark the direction of the current in the circuit on Fig. 3.1. Label your arrow I . Give a reason for your choice.

.....
 [2]

3 Calculate the terminal p.d. V_{XY} between X and Y during the charging process.

$V_{XY} = \dots\dots\dots$ V [2]

4 Show that the mean rate of increase of energy stored in the cell during the charging process is about 0.7 J s^{-1} .

[2]

(c) A 6.0V 2.0W filament lamp has a resistance of 18Ω when lit to normal brightness. It is connected in series to four 1.5V cells each of internal resistance 0.90Ω .

(i) Explain, using calculations, why the lamp does not light to normal brightness.

[3]

(ii) It is found that by adding more cells in series it is possible to make the lamp light to normal brightness. Calculate the total number of cells needed in the circuit for this to occur. Show your working clearly.

number of cells = [2]

Question	Answer	M	Guidance
3			
a	i	C1 A1 B1	accept 7560 or 7570
	ii 1,2	M1 A1	positive plus correct direction of arrow for first mark; do not penalise if arrow not labelled I. allow (conventional) current is from positive to negative ; or electron flow from - to + [but current must be clockwise in 1]
	3	C1 A1	accept 1.905 or 1.91
	4	C1 A1	allow QV/t with ecf a(i) if necessary (11340/16800) allow 0.7 as final line if 0.675 appears above
b		B1 B1 B1 B1 B1	QWC last marking point needed for full marks allow use (digital) voltmeter across <u>unloaded</u> cell to find E; add R and find one value of V and I; then use equation to find r (points 2 to 5) ignore sign of gradient in determining r allow for no graph plot, using 2 pairs of values of V and I substituted into equation allows r and E to be found.(points 2 to 5)
c	i	B1 B1 B1	allow AW such as: 6 V but total R now 21.6 Ω ; 6 V across 21.6 Ω gives 5 V across 18 Ω ; requires 6 V to light normally allow $P = 1.(6)7$ W for 2 marks; only give the third mark if P labelled as power delivered by cell
	ii	M1 A1	alt: lamp needs $V = 6V$ and $I = 0.33$ A terminal p.d per cell is $1.5 = V + 0.9 \times 0.33$ giving $V = 1.2$ V so $n = 6/1.2 = 5$ allow trial and error method but working must be shown to score any marks
	Total question 3	19	

- 2 (a) A battery of e.m.f. E and internal resistance r delivers a current I to a circuit of resistance R .

Write down an equation for E in terms of r , I and R .

..... [1]

- (b) A 'flat' car battery of internal resistance 0.06Ω is to be charged using a battery charger having an e.m.f. of 14V and internal resistance of 0.74Ω , as shown in Fig. 2.1.

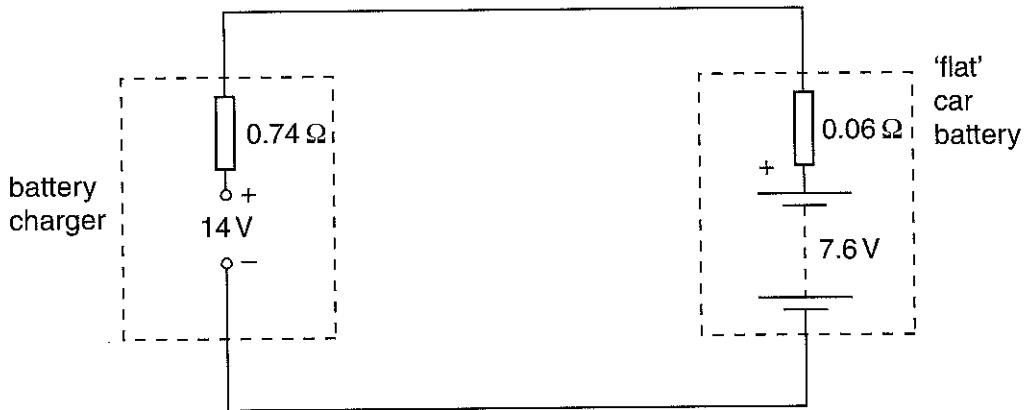


Fig. 2.1

You can see that the battery to be charged has its positive terminal connected to the positive terminal of the battery charger.

At the beginning of the charging process, the e.m.f. of the 'flat' car battery is 7.6V .

- (i) For the circuit of Fig. 2.1, determine

- 1 the total resistance

resistance = Ω [1]

- 2 the sum of the e.m.f.s in the circuit.

e.m.f. = V [1]

- (ii) State Kirchhoff's second law.

.....
 [1]

(iii) Apply the law to this circuit to calculate the initial charging current.

current = A [2]

(c) For the majority of the charging time of the car battery in the circuit of Fig. 2.1, the e.m.f. of the car battery is 12V and the charging current is 2.5A. The battery is charged at this current for 6.0 hours. Calculate, for this charging time,

(i) the charge that passes through the battery

charge = C [2]

(ii) the energy supplied by the battery charger of e.m.f. 14V

energy = J [2]

(iii) the percentage of the energy supplied by the charger which is dissipated in the internal resistances of the battery charger and the car battery.

percentage of energy = % [2]

[Total: 12]

Question		Expected Answers	Marks	Additional Guidance
2	(a)	$E = I(R + r)$	B1	
	(b)	(i) 1 2 0.80 Ω 6.4 V	B1 B1	
	(ii)	(sum of) e.m.f.s = sum /total of p.d.s/sum of voltages (in a loop)	B1	
	(iii)	$6.4 = 0.80I$ $I = 8.0 \text{ A}$	C1 A1	can be 2 ecf from (b)(i), eg $21.6/0.8 = 27 \text{ A}$ (1 ecf) or $21.8/0.68 = 31.8 \text{ A}$ (2 ecf)
	(c)	(i) $Q = It = 2.5 \times 6 \times 60 \times 60$ $= 54000 \text{ (C)}$	C1 A1	allow 1 mark if forgets one or two 60's giving 900 C or 15 C
	(ii)	energy = $QE = 54000 \times 14$ $= 756000 \text{ (J)}$	C1 A1	allow (use of 12 V gives) 648000 J for 1 mark
	(iii)	energy loss = $I^2Rt = VIt = 2 \times 2.5 \times 6.0 \times 60 \times 60 = 108000 \text{ J}$ percentage = $(108000/756000) \times 100 = 14\%$	C1 A1	accept $Q\Delta V = 54000 \times 2.0 = 108000 \text{ J}$ accept $Q\Delta V/QE = 2.0/14.0 = 14\%$ not $756000/54000 = 14\%$
Total question 2			12	