



A Level Physics Exam Packs

Capacitors

Name:

Form:

Question	Mark

Answer **all** the questions.

1 (a) Define *capacitance*.

.....
 [1]

(b) Fig. 1.1 shows a circuit consisting of a resistor and a capacitor of capacitance $4.5\ \mu\text{F}$.

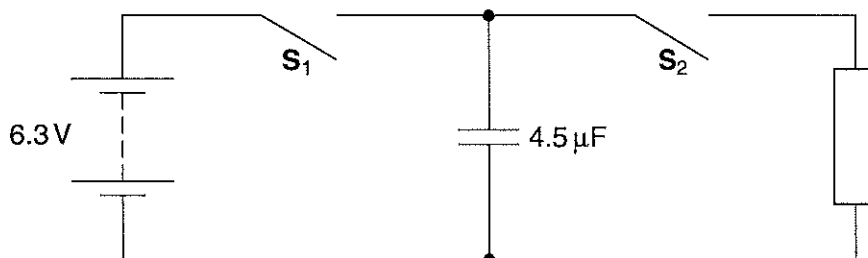


Fig. 1.1

Switch S_1 is closed and switch S_2 is left open. The potential difference across the capacitor is 6.3V .

Calculate

(i) the charge stored by the capacitor

charge = μC [1]

(ii) the energy stored by the capacitor.

energy = J [2]

(c) Switch S_1 is opened and switch S_2 is closed.

(i) Describe and explain in terms of the movement of electrons how the potential difference across the capacitor changes.

.....

 [3]

(ii) The energy stored in the capacitor decreases to zero. State where the initial energy stored in the capacitor is dissipated.

.....
 [1]

(d) Fig. 1.2 shows the $4.5\ \mu\text{F}$ capacitor now connected in parallel with a capacitor of capacitance $1.5\ \mu\text{F}$. Both switches are open and both capacitors are uncharged.

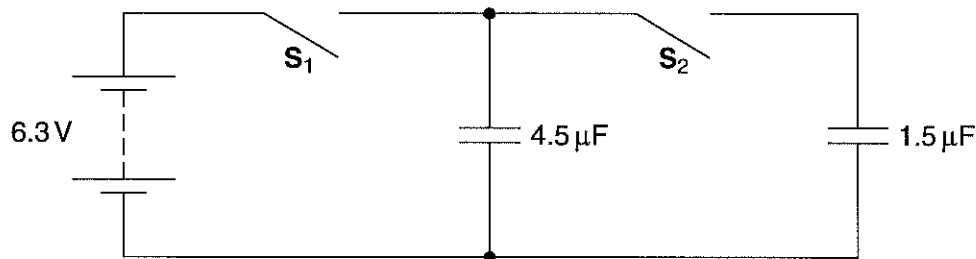


Fig. 1.2

Switch S_1 is closed. The potential difference across the $4.5\ \mu\text{F}$ capacitor is now 6.3V. Switch S_1 is opened and then switch S_2 is closed.

(i) Calculate the total capacitance of the circuit when S_2 is closed.

capacitance = μF [1]

(ii) Calculate the final potential difference across the capacitors.

potential difference = V [2]

[Total: 11]
 Turn over

Question	Expected Answers	Marks	Additional Guidance
1 a	Capacitance = charge per (unit) potential difference	B1	Allow: capacitance = charge / potential difference, charge/pd, charge/voltage but not charge / volt, coulomb /pd (no mixture of quantities and units. Allow 'over' instead of per
b (i)	$Q = CV = 4.5 \mu \times 6.3 = 28.35 \mu\text{C}$	B1	Allow: 28 (≥ 2 sf)
(ii)	$E = \frac{1}{2} CV^2 = 0.5 \times 4.5 \times \mu \times (6.3)^2$ $= 8.9(3) \times 10^{-5} \text{ (J)} / 89.3 \mu\text{(J)}$	C1 A1	Allow use of $E = \frac{1}{2} QV$ and the Q value from (b)(i) $Q=28$ $E= 8.82$ and $Q=28.4$ $E=8.946$ Allow ecf from (b)(i) penalise power of ten error (-1)
c (i)	Electrons / they move in an anticlockwise direction Charge on plates decreases / electrons neutralise positive charge p.d. decreases <u>exponentially</u>	B1 B1 B1	Alternatives for anticlockwise: from / lower plate around the circuit, from / lower plate through the resistor to top plate implied Capacitor discharges / loses charge
(ii)	(dissipated as heat) in the resistor / wires	B1	
d (i)	Total capacitance = $1.5 + 4.5 = 6(.0) \mu\text{F}$	A1	Allow one SF
(ii)	Original charge on $4.5 \mu\text{F}$ capacitor is conserved ($28.35 \mu\text{C}$) $V = (28.35 \mu) / (1.5 + 4.5) \mu = 4.7 \text{ (V)}$	C1 A1	ecf from (b)(i) and (d)(i)
	Total	[11]	

2 (a) Define *capacitance*.

.....
 [1]

(b) Fig. 2.1 shows two capacitors of capacitance $150\ \mu\text{F}$ and $450\ \mu\text{F}$ connected in series with a battery of e.m.f. 6.0V . The battery has negligible internal resistance.

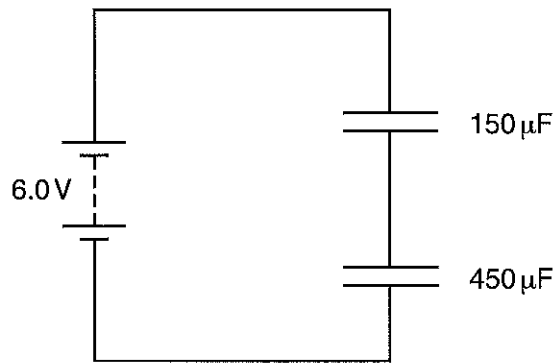


Fig. 2.1

For the circuit shown in Fig. 2.1, calculate

(i) the potential difference across the $150\ \mu\text{F}$ capacitor

potential difference = V [2]

(ii) the charge stored by the $150\ \mu\text{F}$ capacitor

charge = C [1]

(iii) the total capacitance of the circuit.

capacitance = F [1]

- (c) The fully charged capacitors shown in (b) are disconnected from the battery. The capacitors are then connected in series with a resistor R of resistance $45\text{ k}\Omega$ and an open switch S as shown in Fig. 2.2.

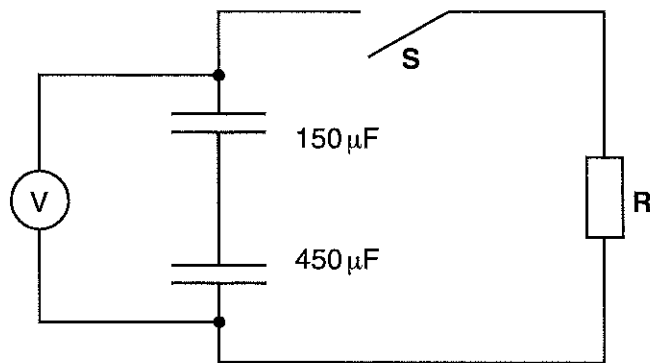


Fig. 2.2

The p.d. V across the capacitors is measured with a voltmeter of infinite resistance. The switch S is closed at time $t = 0$ and measurements of V are made at regular time intervals.

- (i) Show that the time constant for the circuit is about 5s.

[1]

- (ii) On Fig. 2.3 sketch the variation of p.d. V with time t .

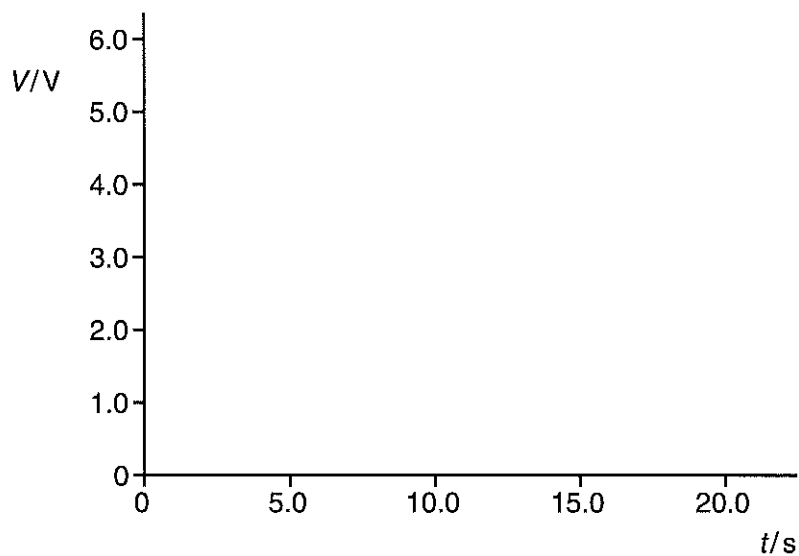


Fig. 2.3

[3]

(iii) At time $t = 0$ calculate the ratio

$$\frac{\text{energy stored by the } 150 \mu\text{F capacitor}}{\text{energy stored by the } 450 \mu\text{F capacitor}}$$

ratio = [2]

(iv) State and explain how the ratio varies with time.

.....
.....
..... [2]

[Total: 13]

Question	Expected Answers	Marks	Additional guidance
2 (a)	capacitance = charge / potential difference	B1	Allow: p.d. and voltage Not: charge per volt or coulombs per p.d
(b) (i)	$V = Q/C$ and $Q = \text{constant}$ in series circuit $V = \frac{450}{450+150} \times 6.0$ potential difference = 4.5 (V)	C1 A1	Allow: 1 mark for an answer of 1.5 (V) Note: Using (b)(i), alternative marking scheme $V = 6.75 \times 10^{-4} / 150 \times 10^{-6}$ C1 $V = 4.5$ V A1
(b) (ii)	charge = $150 \times 10^{-6} \times 4.5$ charge = 6.75×10^{-4} (C)	B1	Possible e.c.f. Note: Using (b)(iii) ... $Q = 6.0 \times 1.125 \times 10^{-4} = 6.75 \times 10^{-4}$ (C)
(b) (iii)	$\frac{1}{C} = \frac{1}{150} + \frac{1}{450}$ (working in μF) capacitance $C_T = 1.125 \times 10^{-4}$ (F) or 113 μF	B1	Possible alternative: capacitance = $6.75 \times 10^{-4} / 6.0$ capacitance = 1.125×10^{-4} (F) or 113 μF Possible e.c.f. from (ii)
(c) (i)	time constant = CR time constant = $1.125 \times 10^{-4} \times 45 \times 10^3$ time constant = 5.06 (s)	M1 A0	Note: The mark is for multiplying correct C and R values Possible e.c.f. from (b)(iii)
(c) (ii)	Graph starting from 6.0 (V) Correct shaped curve Approximately correct value of V at CR	B1 B1 B1	Note: The (exponential decay) curve must not touch or cut the time axis Note: V is 2 to 2.5 (V) at $t \approx 5$ s

Question	Expected Answers	Marks	Additional guidance
(iii)	$\frac{1}{2} \times 4.5^2 \times 150 \times 10^{-6}$ and $\frac{1}{2} \times 1.5^2 \times 450 \times 10^{-6}$ $\text{ratio} = \frac{0.5 \times 4.5^2 \times 150 \times 10^{-6}}{0.5 \times 1.5^2 \times 450 \times 10^{-6}}$ $\text{ratio} = 3$ <p style="text-align: center;">Or</p> $\frac{1}{2} Q^2 / C_{150}$ and $\frac{1}{2} Q^2 / C_{450}$ $\text{ratio} = C_{450} / C_{150}$ $\text{ratio} = 3$	C1 A1 C1 A1	Allow: with or without the 10^{-6} Possible e.c.f. from (b)(i) and (b)(ii) Allow: full credit for correct use of either $\frac{1}{2} QV$ or $\frac{1}{2} Q^2 / C$
(iv)	The ratio remains constant The charge / Q is the same for both capacitors	B1 B1	
Total		13	

2 (a) Define the *farad*.

..... [1]

(b) Fig. 2.1 shows a capacitor **C** of capacitance 5.4 nF connected to a battery. The switch **S₁** is closed and the capacitor is charged to a p.d. of 12V.

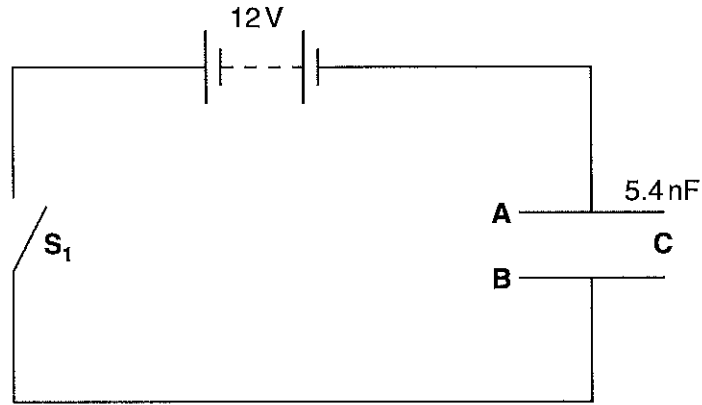


Fig. 2.1

The plates of the capacitor are labelled **A** and **B**.

(i) Explain how the plates of the capacitor become charged in terms of the movement of charged particles in the circuit.

.....

 [2]

(ii) Calculate

1 the charge stored by the capacitor

charge = C [1]

2 the energy transferred to the capacitor.

energy = J [1]

(c) Fig. 2.2 shows the capacitor **C** connected to a resistor **R**.

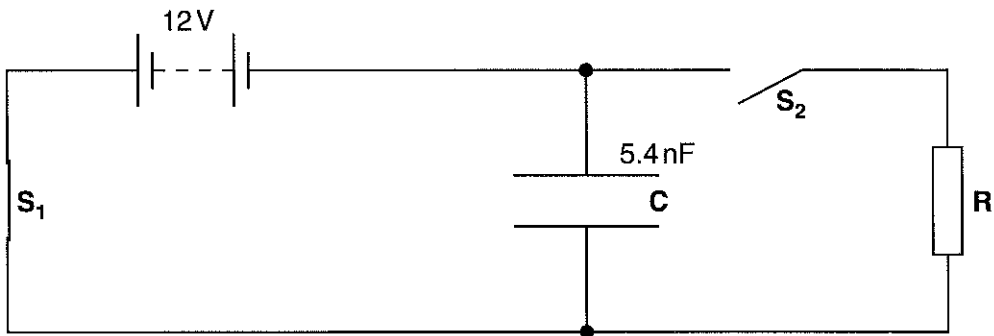


Fig. 2.2

The switch **S₁** is now opened and switch **S₂** is closed. The current in the resistor **R** is monitored. The initial current through **R** is $3.24 \mu\text{A}$.

(i) Show that the resistance of the resistor **R** is $3.7 \text{ M}\Omega$.

[1]

(ii) Calculate the current through **R** after a time $t = 0.080 \text{ s}$.

current = μA [2]

(d) Explain the effect on the initial rate of discharge of the capacitor when a second resistor of resistance $3.7 \text{ M}\Omega$ is connected in parallel with the resistor **R**.

.....

.....

.....

..... [2]

Total: [10]

Question	Expected Answer	Mark	Additional Guidance
2 (a)	coulomb <u>per</u> volt	B1	Allow: 1 F = 1 $\underline{CV^{-1}}$
(b) (i)	<u>Electrons</u> flow 'clockwise' / negative to positive These are deposited on (plate) A (and hence becomes negatively charged) or These are removed from (plate) B (and hence become positively charged)	B1 B1	Not: A becomes negative / B becomes positive
(ii)1	$Q = C \times V = 5.4 \times 10^{-9} \times 12$ charge = 6.48×10^{-8} (C)	B1	
(ii)2	energy = $\frac{1}{2}V^2C = \frac{1}{2} \times 12^2 \times 5.4 \times 10^{-9}$ energy = 3.89×10^{-7} (J)	B1	Possible ecf if Q used from (ii)1
(c) (i)	$R = \frac{12}{3.24 \times 10^{-6}}$ resistance = 3.7×10^6 (Ω)	M1 A0	Allow: 'R = 12/3.24 μ ' (= 3.7 M Ω)
(ii)	time constant = $CR = 5.4 \times 10^{-9} \times 3.7 \times 10^6$ or 0.02 (s) $I = I_0 e^{-t/CR} = 3.24 \times e^{-(0.080/0.020)}$ current = 0.059 (μ A)	C1 A1	Allow: ecf for time constant Allow: 1 mark for 5.9×10^{-11}
(d)	(Total) resistance of circuit <u>halved</u> / time constant is <u>halved</u> Rate of discharge is <u>doubled</u> / (initial) current is <u>doubled</u>	B1 B1	
	Total	10	

Answer **all** the questions.

- 1 (a) Fig. 1.1 shows a circuit consisting of two parallel plates **A** and **B** connected to a high voltage power supply.

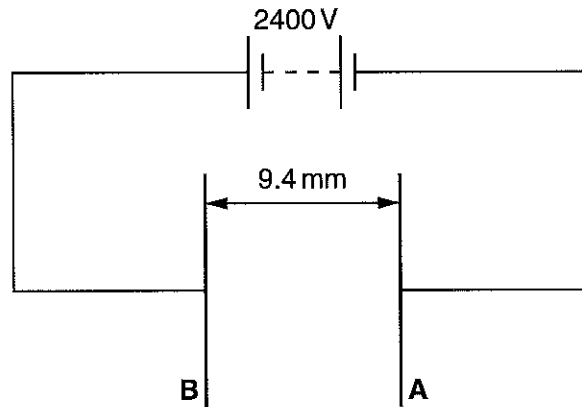


Fig. 1.1

The separation of the plates is 9.4 mm and the p.d. across the plates is 2400 V. There is a vacuum between the plates. Electrons are accelerated from plate **A** to plate **B**.

Calculate

- (i) the force acting on an electron when it is between the plates

force = N [2]

- (ii) the gain in kinetic energy of an electron when it travels from **A** to **B**

kinetic energy = J [2]

- (iii) the speed of the electron when it reaches plate **B**. Assume that the speed of the electron is initially zero at plate **A**.

speed = m s^{-1} [1]

3

- (b) The separation between the plates is doubled but the p.d. across the plates is kept the same. Explain how this would affect the answer to (a)(ii).

.....

.....

.....

..... [2]

[Total: 7]

Question			Expected Answer	Mark	Additional Guidance
1	(a)	(i)	$E = \frac{V}{d} = \frac{2400}{9.4 \times 10^{-3}}$ $E = 2.55 \times 10^5 \text{ (V m}^{-1}\text{)}$ force = $E \times Q = 2.55 \times 10^5 \times 1.60 \times 10^{-19}$ force = 4.09×10^{-14} (N)	C1 A1	Allow 1 mark for 4.1×10^{-14} , $n \neq 14$ Allow 2sf answer of 4.1×10^{-14} (N) Alternative: $F = \frac{Ve}{d} = \frac{2400 \times 1.60 \times 10^{-19}}{9.4 \times 10^{-3}}$ C1 force = $4.08(5) \times 10^{-14}$ (N) A1 [Allow: 4.08×10^{-14} (N)]
		(ii)	$\text{KE} = e \times V \quad \text{or} \quad \text{KE} = F \times d$ $\text{KE} = 1.6 \times 10^{-19} \times 2400 \quad \text{or} \quad \text{KE} = 4.09 \times 10^{-14} \times 9.4 \times 10^{-3}$ $\text{KE} = 3.84 \times 10^{-16} \text{ (J)}$	C1 A1	Allow 2 sf answer Possible ecf if answer from (a)(i) is used
		(iii)	$\text{KE} = \frac{1}{2}mv^2$ $v = \sqrt{\frac{2 \times 3.84 \times 10^{-16}}{9.11 \times 10^{-31}}}$ speed = $2.9(0) \times 10^7 \text{ (m s}^{-1}\text{)}$	B1	Possible ecf if answer from (a)(ii) is used
	(b)		There is no change (to the gain in KE) work done or $\text{KE} = Fd$, F or E is halved <u>and</u> d is doubled or work done or $\text{KE} = VQ$ and V is the same or work done or $\text{KE} = VQ$ and this does not depend on distance	M1 A1	
Total				7	

Answer **all** the questions.

1 (a) Capacitance is measured in farads. Define the *farad*.

.....
..... [1]

(b) Fig. 1.1 shows the graph of potential difference V against charge Q stored for a capacitor of capacitance C .

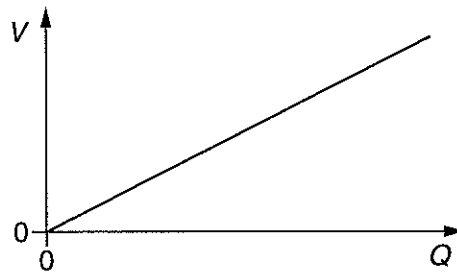


Fig. 1.1

State the quantity represented by the

(i) gradient of the graph

..... [1]

(ii) area under the graph.

..... [1]

- (c) You are given three capacitors of capacitances $100\mu\text{F}$, $200\mu\text{F}$ and $500\mu\text{F}$. Calculate the **minimum** total capacitance of these three capacitors in a combination. Show how the capacitors are connected.

capacitance = μF [3]

- (d) A 0.10F capacitor is charged at a constant rate with a **steady current** of 40mA for a time of 60s . Calculate the final

- (i) charge stored by the capacitor

charge = C [2]

- (ii) energy stored by the capacitor.

energy = J [2]

[Total: 10]

Note about significant figures:

If the data given in a question is to 2 sf, then allow answers to 2 or more sf.
 If an answer is given to fewer than 2 sf, then penalise once only in the entire paper.
 Any exception to this rule will be mentioned in the Guidance.

Question	Answer	Marks	Guidance
1 (a)	(farad = 1) coulomb per (unit) volt	B1	Allow: C V ⁻¹
(b) (i)	1/C	B1	Allow: 'inverse of C'
(b) (ii)	work (done) / energy	B1	
(c)	<p>Diagram: All 3 capacitors connected in series</p> $\frac{1}{C} = \frac{1}{100} + \frac{1}{200} + \frac{1}{500} \quad / \quad \frac{1}{C} = 1.7 \times 10^{-2}$ <p>capacitance = 59 (μF)</p>	B1 C1 A1	<p>Note: Correct symbol must be used for capacitor and at least one of the capacitance values (without the unit) must be shown</p> <p>Allow: Answer to 1 sf Note: Answer to 3sf is 58.8 (μF) Allow: 1.7 × 10⁻² (μF) scores 1 mark from the C1A1</p>
(d) (i)	Q = 0.040 × 60 charge = 2.4 (C)	C1 A1	Allow: 1 mark for 2.4 × 10 ⁰ , n ≠ 0 (POT error)
(d) (ii)	$\text{energy} = \frac{1}{2} \times \frac{2.4^2}{0.10}$ <p>energy = 29 (J)</p>	C1 A1	<p>Possible ecf from (d)(i)</p> <p>Note: Answer to 3 sf is 28.8 (J) Allow full credit for correct use of ½ VQ or ½ V²C; the final p.d is 24 (V)</p>
	Total	10	

- 4 (a) Define *capacitance*.

.....
 [1]

- (b) Fig. 4.1 shows an arrangement of three identical capacitors connected to a 6.0V battery.

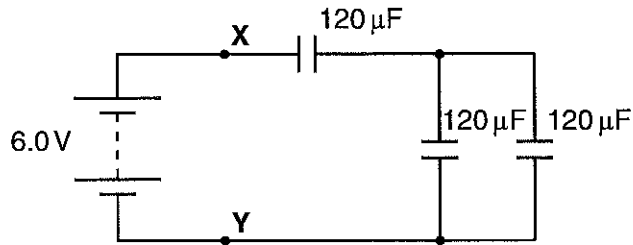


Fig. 4.1

Each capacitor has a capacitance of $120\ \mu\text{F}$.

- (i) Show that the total capacitance of the circuit is $80\ \mu\text{F}$.

[2]

- (ii) Calculate the total energy stored by the capacitors.

energy = J [2]

- (iii) The battery is disconnected from the circuit shown in Fig. 4.1. The p.d. between points X and Y remains at 6.0V. A fixed resistor of resistance R is now connected between X and Y. Fig. 4.2 shows the variation of the p.d. V across the resistor with time t .

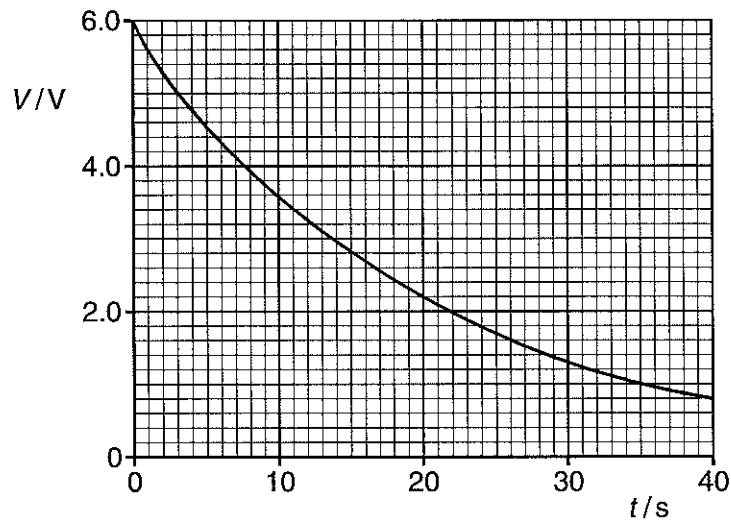


Fig. 4.2

- 1 Use Fig. 4.2 to show that the circuit has a time constant of 20s.

[1]

- 2 Hence, calculate the resistance R of the resistor.

$R = \dots\dots\dots \Omega$ [2]

[Total: 8]

Question		Answers	Marks	Guidance
4	(a)	capacitance = charge/p.d. or capacitance = charge per (unit) p.d.	B1	Allow: voltage instead of p.d. Note: Do not allow mixture of quantity and unit, e.g. 'charge per (unit) volt'
	(b) (i)	$C_{\text{parallel}} = 240 \text{ } (\mu\text{F})$ $C_T = (240 \times 120)/(240 + 120)$ or $C_T = (240^{-1} + 120^{-1})^{-1}$ total capacitance = 80 (μF)	C1 C1 A0	Allow : 1 mark if C_T is not the subject, e.g: $\frac{1}{C_T} = \frac{1}{240} + \frac{1}{120}$
	(ii)	$E = \frac{1}{2} V^2 C$ $E = \frac{1}{2} \times 6.0^2 \times 80 \times 10^{-6}$ energy = 1.4×10^{-3} (J) or 1.44×10^{-3} (J)	C1 A1	Possible ecf Allow: 1 mark for an answer 1.44×10^n ($n \neq -3$)
	(iii)1	$6.0/e = 2.2$ (V) (as on graph) Or $6.0 \times 0.37 = 2.2$ (V) (as on graph) Or At 20 (s), $V = 2.2$ (V), $2.2/6.0 = 0.37$ (or e^{-1})	B1	Allow: Graph reading within ± 0.2 V
	(iii)2	$CR = 20$ $R = \frac{20}{80 \times 10^{-6}}$ $R = 2.5 \times 10^5$ (Ω)	C1 A1	Allow: Follow through with CR value from (iii)1
Total			8	

- 2 On Fig. 1.2, sketch a graph to show the variation of potential difference V across the capacitor with time t .

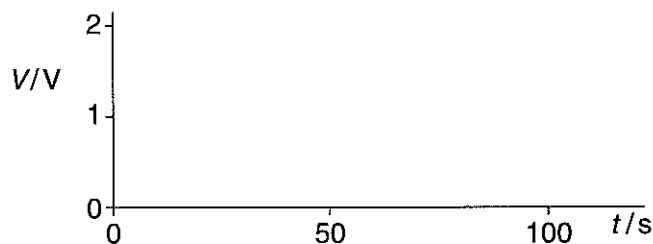


Fig. 1.2

[2]

- (b) Fig. 1.3 shows an arrangement used to determine the speed of a bullet.

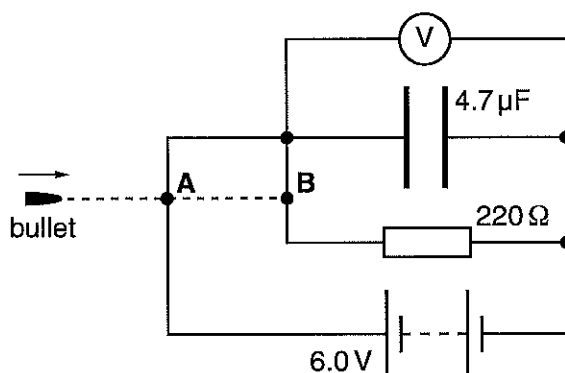


Fig. 1.3

The value of the resistance of the resistor and the value of the capacitance of the capacitor are shown in Fig. 1.3. The voltmeter reading is initially 6.0V. The bullet first breaks the circuit at **A**. The capacitor starts to discharge **exponentially** through the resistor. The capacitor stops discharging when the bullet breaks the circuit at **B**. The final voltmeter reading is 4.0V.

- (i) Calculate the time taken for the bullet to travel from **A** to **B**.

time = s [3]

- (ii) The separation between **A** and **B** is 0.10m. Calculate the speed of the bullet.

speed = ms^{-1} [1]

[Total: 11]

Turn over

Question			Answer	Marks	Guidance
1	(a)	(i)	Any <u>two</u> from: Correct direction of movement of electrons Electrons deposited on Y / removed from X An equal number of electrons removed and deposited on plates (AW)	B1 × 2	
		(ii)1	$Q = 40 \times 10^{-6} \times 100 (= 4.0 \times 10^{-3} \text{ C})$ $4.0 \times 10^{-3} = 1.6 \times C$ $C = 2.5 \times 10^{-3} \text{ (F)}$	C1 C1 A1	Allow: 2 marks for $2.5 \times 10^n \text{ (F)}$, where $n \neq -3$ (POT error)
		(ii)2	Graph starts at <u>origin</u> and has positive gradient A straight line graph that passes between 1-2 V at 100 s	M1 A1	
	(b)	(i)	$CR = 4.7 \times 10^{-6} \times 220 (= 1.03 \times 10^{-3} \text{ s})$ $4.00 = 6.00e^{-\frac{t}{1.03 \times 10^{-3}}}$ $t = -\ln(4.00/6.00) \times 1.03 \times 10^{-3}$ time = $4.2 \times 10^{-4} \text{ (s)}$	C1 C1 A1	Note: Answer to 3 sf is $4.19 \times 10^{-4} \text{ (s)}$ Allow: 2 marks for $t = -\ln(4.00/6.00) \times 1.03 \times 10^{-3} = 1.8 \times 10^{-4} \text{ s}$
		(ii)	speed = $\frac{0.100}{4.2 \times 10^{-4}}$ speed = $240 \text{ (m s}^{-1}\text{)}$	B1	Possible ecf from (b)(i)
Total				11	

Answer **all** the questions.

- 1 (a) Fig. 1.1 shows an arrangement of capacitors.

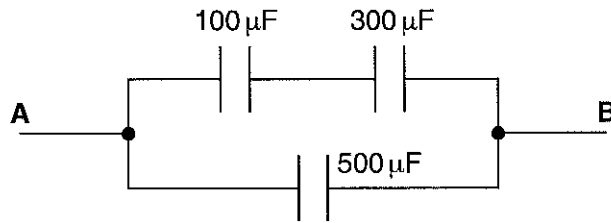


Fig. 1.1

Determine the total capacitance between **A** and **B**.

capacitance = μF [2]

- (b) A capacitor of capacitance $500\ \mu\text{F}$ is charged to 6.0V . A student places her thumb and first finger across the terminals of the capacitor as shown in Fig. 1.2. This provides a high resistance path across the terminals of the capacitor causing it to discharge.

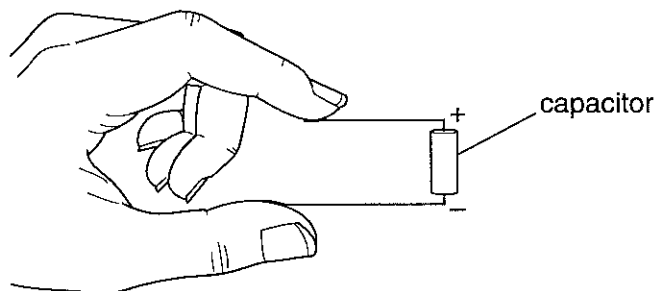


Fig. 1.2

Fig. 1.3 shows the variation of potential difference V across the capacitor with time t .

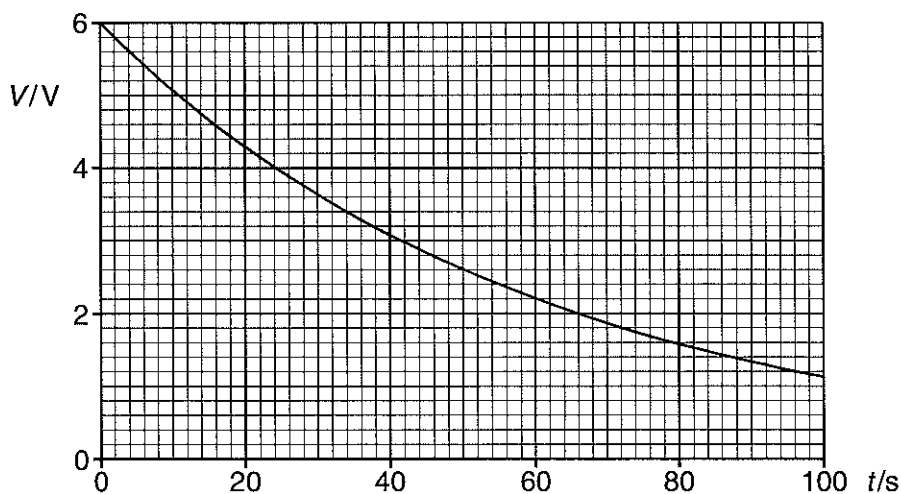


Fig. 1.3

(i) Use Fig. 1.3 to calculate the resistance across the terminals of the capacitor.

resistance = Ω [3]

(ii) Calculate the energy lost by the capacitor from time $t = 0$ to $t = 30$ s.

energy lost = J [3]

[Total: 8]

Question	Answer	Marks	Guidance	
1	(a)	Series branch: Using $(100^{-1} + 300^{-1})^{-1}$ and $C = 75 \mu\text{F}$ capacitance = $500 + 75$ capacitance = $575 \mu\text{F}$	C1 A1	Possible ecf, if capacitance of series branch is incorrect
		(b) (i)	<p>Time constant method: 37% of 6.0 V is 2.2 V. The time taken to reach 2.2 V is equal to the time constant</p> <p>time constant = 60 (s) / CR = 60 (s)</p> <p>$500 \times 10^{-6} \times R = 60$</p> <p>$R = \frac{60}{500 \times 10^{-6}}$ resistance = $1.2 \times 10^5 \Omega$</p> <p>Substitution method: Correct values for p.ds and t substituted into $V = V_0 e^{-\frac{t}{CR}}$ Correct values substituted into $\ln(V/V_0) = -\frac{t}{CR}$ resistance = $1.2 \times 10^5 \Omega$</p>	C1 C1 A1 C1 C1 A1
	(ii)	<p>Correct p.ds from graph: 6 (V) and 3.6 (V) $\frac{1}{2} \times 500 \times 10^{-6} \times 6.0^2$ or $\frac{1}{2} \times 500 \times 10^{-6} \times 3.6^2$ energy is 9.00×10^{-3} (J) and 3.24×10^{-3} (J) energy lost = 5.76×10^{-3} (J) or 5.8×10^{-3} (J)</p>	C1 C1 A1	<p>Allow V value to be in the range 3.5 V to 3.7 at 30s</p> <p>Note: Do not penalise 10^0 error from (b)(ii) again here Allow 1 mark for: $\frac{1}{2} \times 500 \times 10^{-6} \times (6.0 - 3.6)^2 = 1.44 \times 10^{-3}$ (J) Note: Do not penalise use of $575 \mu\text{F}$ again. This gives a value of 6.62×10^{-3} (J)</p>
		Total	8	

4 (a) Define the *time constant* of a capacitor-resistor discharge circuit.

.....

 [1]

(b) A student designs a circuit with a time constant of 5.0 s. State suitable values for resistance R and capacitance C for this circuit.

$R =$ $C =$ [1]

(c) Fig. 4.1 shows a circuit with a capacitor of capacitance 0.010 F.

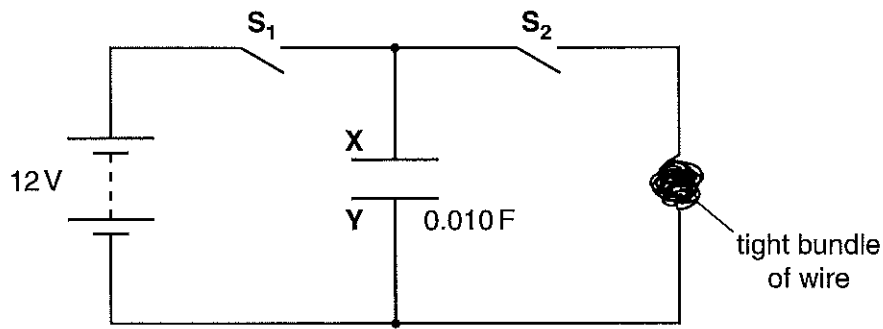


Fig. 4.1

A tight bundle of wire is made from 5.0 m of insulated wire of diameter 0.12 mm and resistivity $4.9 \times 10^{-7} \Omega \text{m}$. The material of the wire has density 8900kg m^{-3} and specific heat capacity $420 \text{J kg}^{-1} \text{K}^{-1}$.

(i) Calculate the time constant of the circuit.

time constant = s [3]

Question	Answers	Marks	Guidance
4	(a)		The time taken for the p.d / current / charge to decrease to 1/e of its (initial) value.
	(b)		Any suitable values with units, eg: 5 M Ω and 1 μ F.
	(c) (i)		$R = \frac{4.9 \times 10^{-7} \times 5.0}{\pi \times (0.06 \times 10^{-3})^2}$ or $R = 217 (\Omega)$ time constant = 0.010×217 time constant = 2.2 (s)
	(ii)		Electrons are removed from X or electrons are deposited on Y.
			X becomes positive or Y becomes negative
			(The size of charge is the same because) an equal number of electrons are removed and deposited (on the plates).
	(iii)		$E = \frac{1}{2} \times 0.010 \times 12^2$ or $E = 0.72$ (J) $m = 8900 \times [\pi \times (0.06 \times 10^{-3})^2 \times 5.0]$ or $5.0(3) \times 10^{-4}$ (kg) $5.03 \times 10^{-4} \times 420 \times \Delta\theta = 0.72$ increase in temperature = 3.4 ($^{\circ}$ C)
	(iv)		Energy or V^2 increases by a factor of 4.
			The (change in temperature) increases by a factor of 4 (because $\Delta\theta \propto E$).
			Total 14

4 (a) A charged capacitor is connected across the ends of a negative temperature coefficient (NTC) thermistor kept at a fixed temperature. The capacitor discharges through the thermistor. The potential difference V across the capacitor is maximum at time $t = 0$.

(i) On the axes of Fig. 4.1, carefully sketch a graph to show how the potential difference V across the capacitor varies with time t . Label this graph L.

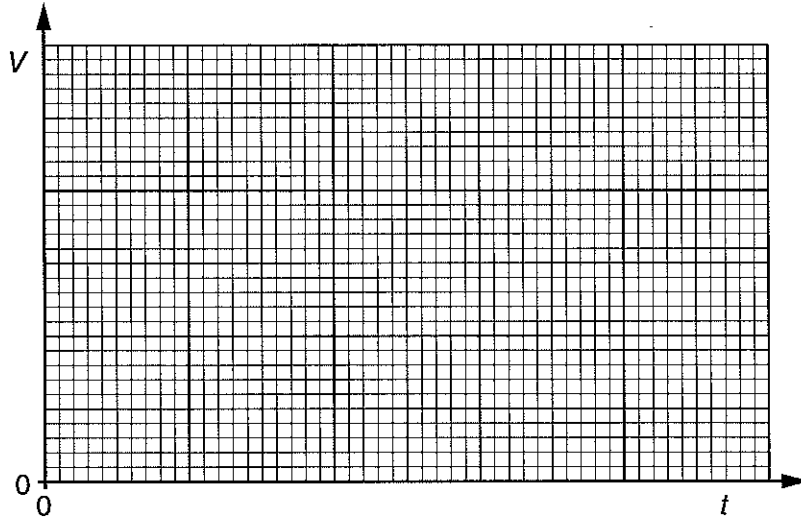


Fig. 4.1

[1]

(ii) The temperature of the thermistor is increased to a higher fixed value. On Fig. 4.1, sketch another graph to show the variation of V with t when the same charged capacitor is discharged across the ends of the hotter thermistor. Label this graph H. [1]

(iii) Explain how you can show that the graph sketched in (i) has a constant-ratio property (exponential decay).

.....

.....

..... [1]

(b) Fig. 4.2 shows an electrical circuit.

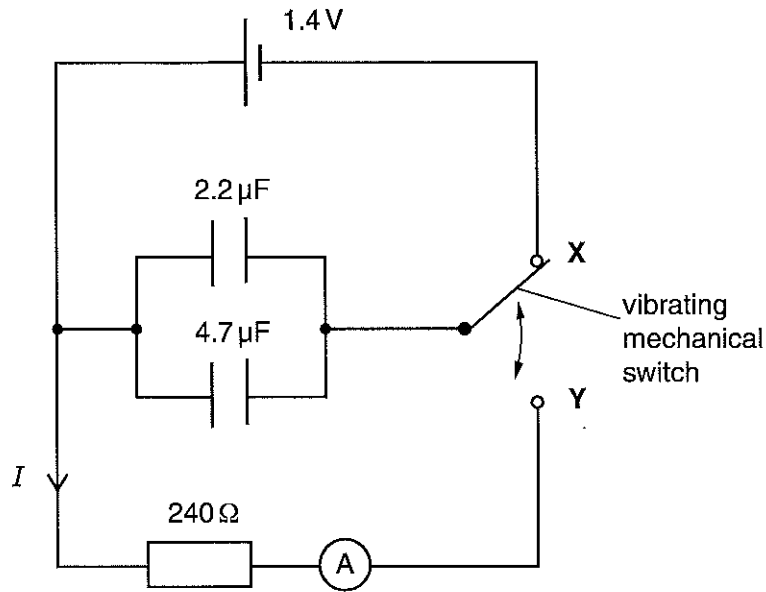


Fig. 4.2

The cell has e.m.f. 1.4V and negligible internal resistance. The values of the capacitors and the resistor are shown in Fig. 4.2. A mechanical switch vibrates between contacts X and Y at a frequency of 120Hz.

(i) Calculate the time constant of the circuit.

time constant = s [1]

(ii) Calculate the value of the average current I in the resistor. Assume that the capacitors are fully discharged between each throw of the switch.

$I =$ A [3]

- (iii) The frequency of vibration of the mechanical switch is doubled. Explain why the average current in the circuit is not doubled.

.....

.....

.....

..... [2]

Question 5 starts on page 12

Question			Answer	Marks	Guidance
4	(a)	(i)	Correct shape of (exponential) decay curve (labelled L)	B1	Note: The curve must show a gradient of decreasing magnitude as time increases and appear to have a finite value of V at $t = 0$ Ignore any levelling of the curve or $V = 0$ towards the end
		(ii)	Correct shape of curve (labelled H)	B1	Note: As (i) and this curve must show a smaller time constant than (i); the initial V can be different Note: One of the curves must be labelled
		(iii)	Correct explanation in terms of constant-ratio for V values for <u>fixed</u> intervals of t	B1	Allow V is halved every half-life; V decreases to 0.37 (of its initial value) after every time constant Note: This can be scored on a suitably labelled sketch graph in either (ii) or Fig. 4.1
(b)	(i)	(i)	(time constant = $6.9 \times 10^{-6} \times 240$) time constant = 1.7×10^{-3} (s)	B1	Note: Answer to 3 sf 1.66×10^{-3} (s)
		(ii)	charge = $6.9 \times 10^{-6} \times 1.4$ (= 9.66×10^{-6} C) ($\Delta t = 1/120 = 0.0083$ s) current = $\frac{6.9 \times 10^{-6} \times 1.4}{0.0083}$ current = 1.2×10^{-3} (A)	C1	Possible ecf from (b)(i) for value of total capacitance
				C1 A1	Note: Answer to 3 sf 1.16×10^{-3} (A) Allow: 2 marks for $9.66 \times 10^{-6} \times 60 = 5.8 \times 10^{-4}$ (A); $\Delta t = 1/60$ s used Allow: 2 marks for $9.66 \times 10^{-6} \times 240 = 2.3 \times 10^{-3}$ (A); $\Delta t = 1/240$ s used
(iii)	The capacitors do not fully discharge (AW) Any <u>one</u> from: <ul style="list-style-type: none"> Period (of switching) is (halved to) 4.2×10^{-3} (s) (and this time is comparable to the time constant) The time constant (of the circuit) and period of mechanical switch are comparable / similar 	B1			
		B1			
Total				9	