

- 3 (a) Kirchhoff's laws can be used to analyse any electrical circuit. State each of Kirchhoff's laws and the physical quantity associated with each law that is conserved in the circuit.

(i) Kirchhoff's first law

.....

.....

.....

.....

.....

..... [2]

(ii) Kirchhoff's second law

.....

.....

.....

.....

.....

..... [2]

- (b) The circuit in Fig. 3.1 consists of a battery of e.m.f. 45V and negligible internal resistance and three resistors.

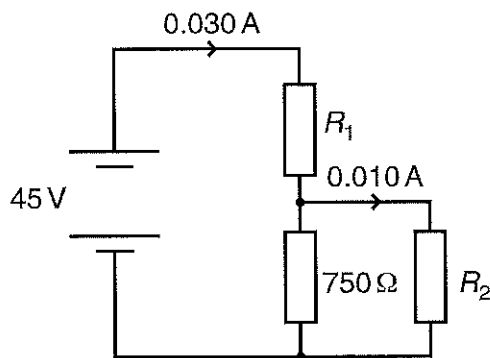


Fig. 3.1

The resistors have resistances R_1 , R_2 and $750\ \Omega$. The current in the resistor of resistance R_1 is 0.030 A. The current in the resistor of resistance R_2 is 0.010 A.

Calculate

- (i) the current I in the $750\ \Omega$ resistor

$$I = \dots\dots\dots \text{ A [1]}$$

- (ii) the p.d. V across the $750\ \Omega$ resistor

$$V = \dots\dots\dots \text{ V [1]}$$

- (iii) the resistances R_1 and R_2 .

$$R_1 = \dots\dots\dots \ \Omega$$

$$R_2 = \dots\dots\dots \ \Omega$$

[2]

Question 3 is continued on page 8

(c) The resistor of resistance R_2 is replaced in Fig. 3.1 by a light dependent resistor (LDR).

(i) Draw the circuit symbol for an LDR on Fig. 3.2 to complete this new circuit.

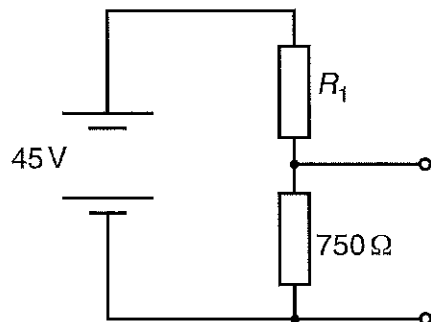


Fig. 3.2

[1]

(ii) The resistance of the LDR falls from about $1.5\text{k}\Omega$ to about 400Ω as the light intensity increases. State and explain, without calculation, how the potential difference across the 750Ω resistor varies as the intensity of the light incident on the LDR increases.

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

[3]

(iii) It is suggested that the LDR in the circuit of Fig. 3.2 is used to monitor changes in the light intensity.

1 Draw a suitable electrical meter in the LDR branch of the circuit on Fig. 3.2 to measure these changes.

2 State the electrical meter that you have chosen and suggest a sensible maximum scale reading.

.....

.....

.....

[3]

[Total: 15]

Question		Answer	Marks	Guidance
3	(a) (i)	<u>sum of/total</u> current into a junction equals the <u>sum of/total</u> current out conservation of charge	B1 B1	total vector sum of currents is zero allow 'point in a circuit' for 'junction'
	(ii)	(sum of) e.m.f.s = <u>sum /total</u> of p.d.s/sum of voltages in/around a (closed) loop (in a circuit) energy is conserved	B1 B1	allow 'in a (closed) circuit' in place of 'loop'
	(b) (i)	current in $750 \Omega = 0.020 \text{ A}$	A1	allow 20 mA or 0.02 A
	(ii)	V across $750 \Omega = 0.02 \times 750 = 15 \text{ V}$	A1	ecf b(i)
	(iii)	$R_1 = (45 - 15)/0.03 = 1000 \Omega$ $R_2 = 15/0.01 = 1500 \Omega$	A1 A1	ecf b(ii)
	(c) (i)	correct symbol connected in circuit	B1	2 arrows pointing towards the resistor at about 45° with or without a circle; arrows outside circle if drawn
A A A	(ii)	<u>total</u> R falls so I <u>in circuit/in</u> R_1 increases so V across R_1 increases <u>and</u> V across 750Ω falls	B1 M1 A1	accept sum of R's in parallel falls R_1 is fixed so V across R_1 increases so V across R's in parallel falls (so V across 750Ω falls) or correct potential divider argument
	(iii)	in series with LDR ammeter (A) 50 mA	in parallel with LDR voltmeter (V) 20 V	M1 A1 B1 allow voltmeter in parallel with R_1 (30 – 50 V) allow multimeter connected as A (series) or V (parallel) and a correct unit for range given allow 20 to 100 mA; or 15 to 50 V
Total			15	

- 3 Fig. 3.1 shows a circuit containing a battery of e.m.f. 12V, two resistors, a light-dependent resistor (LDR), an ammeter and a switch **S**. The battery has negligible internal resistance.

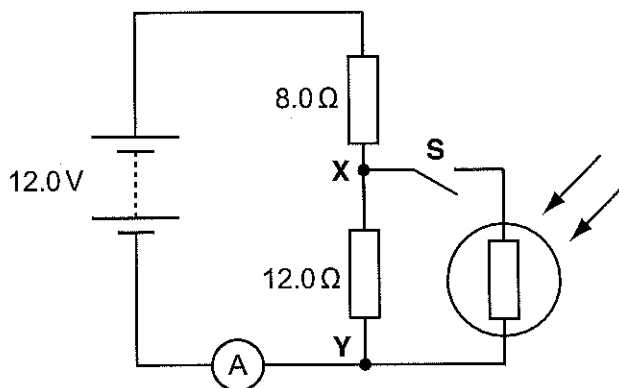


Fig. 3.1

- (a) When the switch **S** is open, show that the potential difference between the points **X** and **Y** is 7.2V.

[2]

- (b) The switch **S** is now closed. Describe and explain the change to each of the following when the intensity of light falling on the LDR is increased:

- (i) the ammeter reading

.....

 [2]

- (ii) the potential difference across **XY**.

.....

 [2]

[Total: 6]

Question		Expected Answers	Marks	Additional Guidance
3				
	a	resistors in series add to 20Ω and current is 0.60 A so p.d. across XY is $0.60 \times 12 (= 7.2 \text{ V})$	B1 B1	accept potential divider stated or formula gives $(12/20) \times 12 \text{ V} (= 7.2 \text{ V})$
	b	i	M1 A1	
		ii	B1 B1	alternative i increases so p.d. across 8.0Ω increases; so p.d. across XY falls
		Total question 3	6	
Question		Expected Answers	Marks	Additional Guidance
4				
	a	i	B1 B1 B1 M1 A1 B1 B1	allow 1.4 to 1.6 V (QWC mark) (alternative QWC mark) max 5 marks which must include at least one of the first 2 marking points
		ii 1 2	B1 C1 A1	apply POT error for 0.083Ω
	b	LED symbol with correct orientation resistor (need not be labelled) and ammeter in series with it voltmeter in parallel across LED only	B1 B1 B1	diode symbol + circle + at least one arrow pointing away
	c	the resistor limits the <u>current</u> in the circuit (when the LED conducts) otherwise it could overheat/burn out/be damaged/AW	B1 B1	
	d	in fig 4.3 the <u>voltage</u> range is from zero to maximum possible in fig. 4.2 the resistance variation is small/AW (so) in fig. 4.2 voltage variation across LED is small	B1 B1 B1	allow 6.0 V accept the LED is part of a potential divider accept only at the top end of the range/AW
		Total question 4	16	

(b) Use Fig. 3.1 to calculate the voltmeter reading when the temperature of the oven is 240°C.

voltmeter reading = V [4]

(c) A light-dependent resistor (LDR) is another component used in sensing circuits.

(i) Complete Fig. 3.3 with an LDR between X and Y.

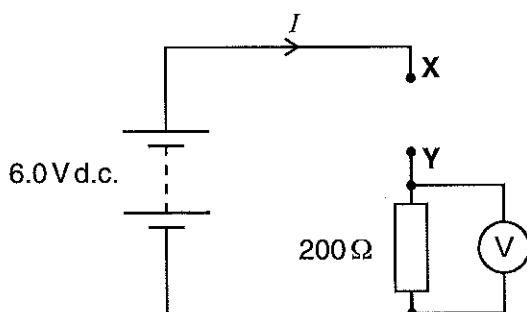


Fig. 3.3

[1]

(ii) State with a reason how the voltmeter reading varies as the intensity of the light incident on the LDR increases.

.....

.....

.....

.....

.....

.....

.....

..... [2]

[Total: 10]

Question		Answer	Marks	Guidance
3 A A A	(a)	R of <u>thermistor</u> decreases as temperature increases supply V is constant/ total R is smaller current increases <u>as</u> $V = IR/AW$	B1 B1 B1	accept more free e's as temperature rises using $I = nAev$ current increases as v decrease very small/AW
	(b)	$R_{th} = 40 \Omega$ at 240°C (stated or used in calculation) total R in circuit = 240Ω $I = 6/240 = 0.025 \text{ A}$ $V = 200 \times 0.025 = 5.0 \text{ V}$	B1 C1 C1 A1	apply ecf if wrong value of R read from graph allow $V = (200/240)6$ so $V = 5.0 \text{ V}$ accept 5 V (no SF error)
	(c) (i)	correct symbol for LDR	B1	no circle required
	(ii)	R of <u>LDR</u> decreases/current in circuit increases so V increases <u>across fixed/200 Ω resistor/AW</u>	M1 A1	accept simple potential divider argument accept voltmeter reading increases
Total			10	

- 3 This question is about the use of a light-dependent resistor (LDR) as a light sensor in a potential divider circuit. Fig. 3.1 shows how the resistance of a particular LDR varies with light intensity.

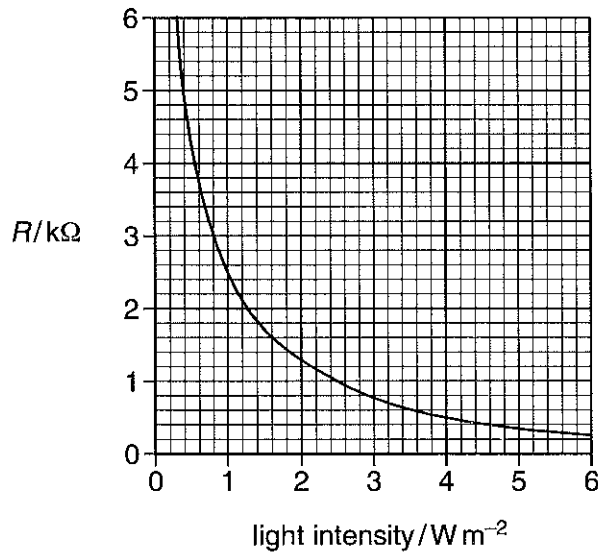


Fig. 3.1

- (a) Explain the term *intensity*.

.....
 [1]

- (b) The intensity of daylight is about $10 W m^{-2}$ and at night time is about $0.1 W m^{-2}$. Describe how the resistance of the LDR changes during the day compared with how it changes at night.

.....

 [2]

- (c) Fig. 3.2 shows a light-sensing potential divider circuit where the LDR is connected in parallel to the input of an electronic circuit that operates a 230V mains lamp.

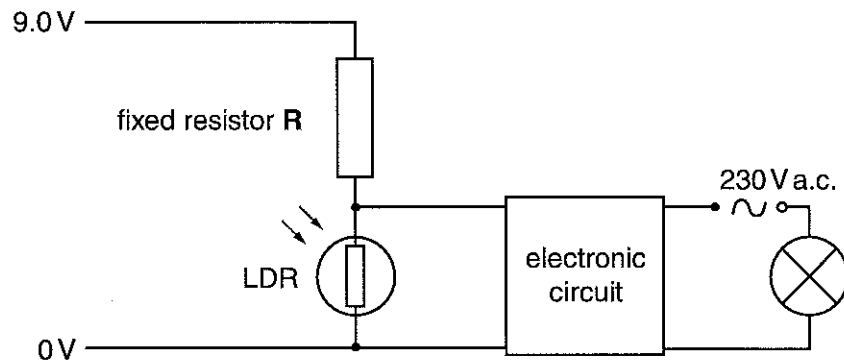


Fig. 3.2

The electronic circuit draws a negligible current. The potential difference across the LDR must be at least 5.0V to activate the circuit and switch on the lamp. The lamp is switched on when the light intensity falls to 1.0W m^{-2} .

- (i) Use Fig. 3.1 to determine the resistance of the LDR at a light intensity of 1.0W m^{-2} .

resistance = $\text{k}\Omega$ [1]

- (ii) Calculate the current in the LDR in Fig. 3.2 for the p.d. across it to be 5.0V.

current = A [2]

- (iii) Show that the resistance of the fixed resistor **R** in Fig. 3.2 is $2.0\text{k}\Omega$.

[1]

- (d) The lamp switches off when the light intensity reaches 2.5W m^{-2} . Calculate the p.d. across the LDR when this happens.

potential difference = V [3]

- (e) Explain why the LDR must be shielded or be at some distance from the lamp when it switches on.

.....
.....
.....
..... [2]

[Total: 12]

Question	Expected Answers	M	Additional Guidance
3			
a	energy per unit area per unit time	B1	accept power per unit area; allow second for unit time
b	Small <u>changes</u> in R for high light intensities/daylight conditions Large <u>changes</u> in R for low light intensities/dim light/night time conditions to change circuit state need a significant change in R to be useful/reliable	B1 B1 B1	accept low R by day, high R by night for 1 mark NOT comparison e.g. R by day smaller than R at night max 2 marks from 3 marking points
c	i 2.5 (k Ω) ii $5.0 = I \times 2.5 \text{ k}\Omega$ giving $I = 2.0 \times 10^{-3} \text{ A}$ iii $4.0 = 2.0 \times 10^{-3} \times R$ or potential divider argument giving $R = 2.0 \times 10^3 \Omega$	A1 C1 A1 M1 A0	allow 2.4 to 2.6 ecf (c)(i) accept 2.0 mA ecf (c)(ii) or ecf (c)(i) accept 2.0 k Ω
d	R (of LDR) = 1.0 (k Ω) potential divider of 1.0 k Ω and 2.0 k Ω giving 3.0 V across LDR	B1 C1 A1	accept $I = 3.0 \text{ (mA)}$ so $V = 3.0 \text{ (mA)} \times 1.0 \text{ (k}\Omega) = 3.0 \text{ V}$
e	light shining on the LDR will cause it to switch the illumination off causing an ON/OFF oscillation/AV	B1 B1	two suitable qualifying statements for the 2 marks
Total question 3		12	

- 5 (a) The circuit in **Fig. 5.1** consists of a d.c. supply of e.m.f. 45 V and negligible internal resistance and three resistors.

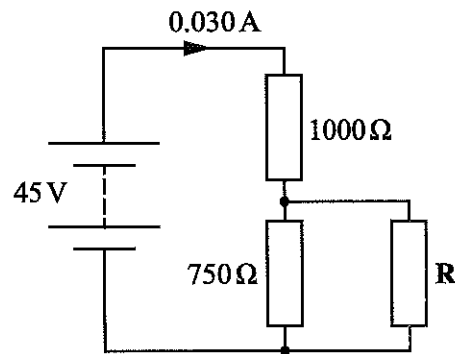


Fig. 5.1

Two of the resistors have resistances 1000 Ω and 750 Ω as shown.

The current drawn from the supply is 0.030 A. Calculate the resistance of **R**.

resistance = Ω [4]

Question	Answer	Marks	Guidance
5 (a)	<p>V across $750 \Omega = 45 - 0.03 \times 1000 = 15$ (V)</p> <p>current in $750 \Omega = 15/750 = 0.02$ (A)</p> <p>current in R = 0.01 (A)</p> <p>$R = 15/0.01 = 1500$ (Ω)</p>	<p>C1</p> <p>C1</p> <p>C1</p> <p>A1</p>	<p>several methods available, e.g.</p> <p>find the total resistance = $45/0.03 = 1500$ (Ω)</p> <p>resistance of parallel pair = 500 (Ω)</p> <p>$R = (500^{-1} + 750^{-1})^{-1} = 1500$ (Ω)</p> <p>or use potential divider argument.</p>
(b)*	<p>Level 3 (5–6 marks) Circuit including meter is correctly drawn. Explanation of action of circuit is correct. Concept of sensitivity understood and 750Ω justified (6 marks)</p> <p>LDR wrong symbol or value of resistor not fully justified (5 marks). <i>There is a well-developed line of reasoning which is clear and logically structured. The information presented is relevant and substantiated.</i></p> <p>Level 2 (3–4 marks) Circuit has correct symbol for LDR Action of circuit explanation limited 750Ω stated but not justified Concept of sensitivity (4 marks)</p> <p>Any point omitted or incorrect (3 marks). <i>There is a line of reasoning presented with some structure. The information presented is in the most-part relevant and supported by some evidence.</i></p>	<p>B1</p> <p>x6</p>	<p>circuit diagram</p> <ol style="list-style-type: none"> resistor and LDR in series ammeter in series or voltmeter in parallel with resistor correct symbols for LDR, ammeter, voltmeter, etc. <p>action of circuit</p> <ol style="list-style-type: none"> when light intensity increases R of LDR falls so I in circuit increases or V across resistor increases or V across LDR decreases (meter reading increases). <p>meter and sensitivity</p> <ol style="list-style-type: none"> need the largest change in current or voltage for a given change in light intensity choose resistor of 750Ω to give the largest change on the meter or need a meter which can display small changes in value of current or voltage.

H156/02

Mark Scheme

June 20XX

Question	Answer	Marks	Guidance
	<p>Level 1 (1–2 marks) Correct symbol for LDR (1 mark) Action of circuit only addresses point (1 mark) Sensitivity poorly addressed (1 mark) (Maximum 2 marks)</p> <p><i>The information is basic and communicated in an unstructured way. The information is supported by limited evidence and the relationship to the evidence may not be clear.</i></p> <p>0 marks No response or no response worthy of credit.</p>		
		Total	10